

How to repair power supply PS5

Breakdown / Troubleshooting

Which tools do you need when fixing power supplies?



Isolator transformer
When you accidentally touch the hot output you will be save



Variable transformer
For testing SMPS from low to high AC voltage

A variable transformer is not a isolator transformer!



Multimeter



Capacitance / ESR meter
To test state of capacitor



Electronic load
To test the secondary output voltage



Oscilloscope
To give a picture of the like PWM signal



Capacitor discharging tool

Safety Guidelines

Electrical Shock


Turn off and unplug power supply when you start repairing.

Wear rubber shoes

If you are tired or want to rush things, don't do that and stop!


Best practice is to assume that the power supply is always ON and LIVE

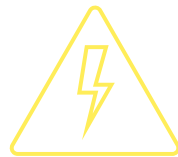Only use plastic screwdrivers when working on the PCB.



Discharge main capacitor

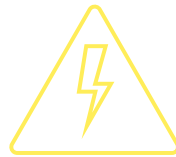
Use a discharging tool to drain the main filter capacitors



Use correct ground

When testing in COLD side use a ground reference on the COLD side.

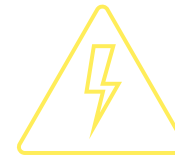When testing in HOT side use a ground reference on the HOT side.




These capacitors can kill you!

Disclaimer – Caution!

Power supplies contain capacitors that can store electrical energy even after the supply is disconnected.

Always assume that capacitors are charged and take appropriate precautions to discharge them before touching or working on the circuit. Use suitable tools, such as insulated discharge probes, and follow recommended safety procedures.

High voltage can be between: 200V - 470V

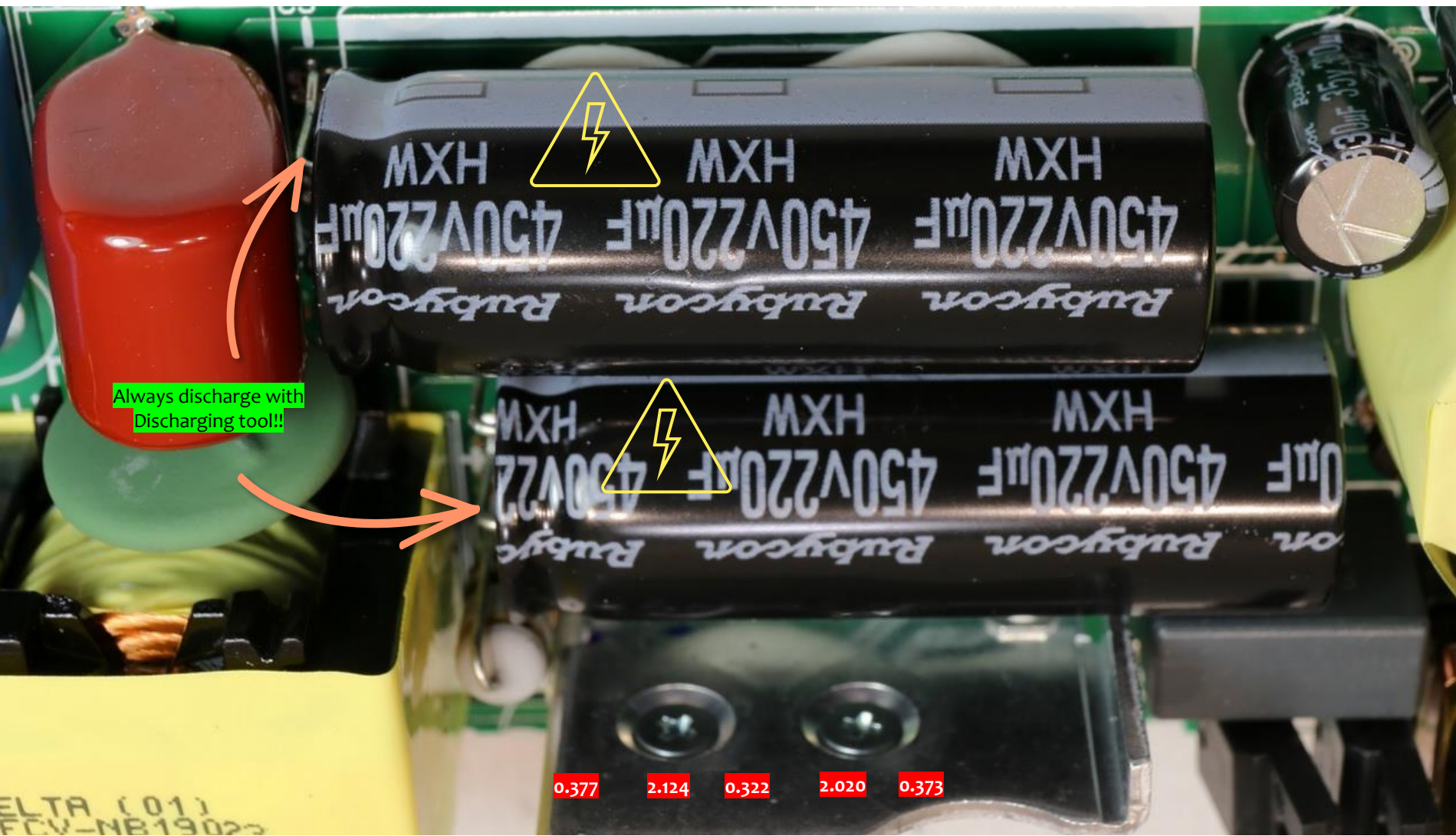


6 common faults with SMPS

1. No power	Symptom	Test
No power	Fuse blown	RFI /EMI circuit APFC circuit LLC circuit
No power	Fuse good	Hot side Cold side




6 common faults with SMPS

2. Low power voltage	Symptom	Test
Output is lower then specified (example: +12V but the output delivers +10V)	No power No standby LED	----

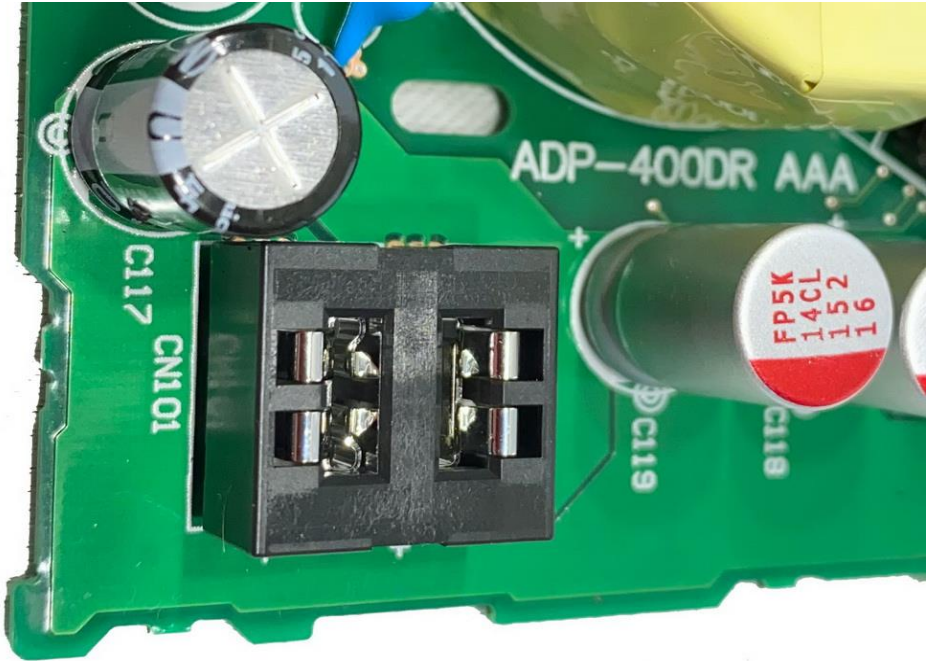

6 common faults with SMPS

3. High power voltage	Symptom	Test
Output is higher then specified (example: +12V but the output delivers +15V)	Power shutdown	----

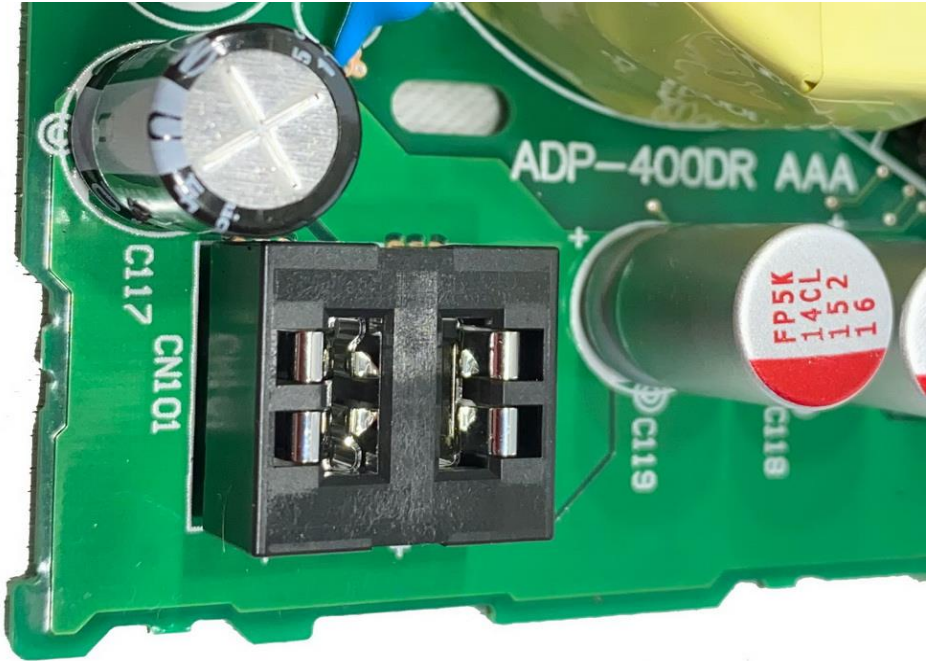


6 common faults with SMPS


4. Power cycling	Symptom	Cause	Test
Output voltage is present then it is turned off and this cycle repeats	The rectifier diodes in the secondary section will produce an voltage that goes high and then low (on / off)	Bad component on secondary side Bad filter capacitors Faulty component in regulation circuit Error detection / feedback circuit Bad component on primary side	Multimeter red probe to cold ground. Red probe to the output of the rectifier diode.



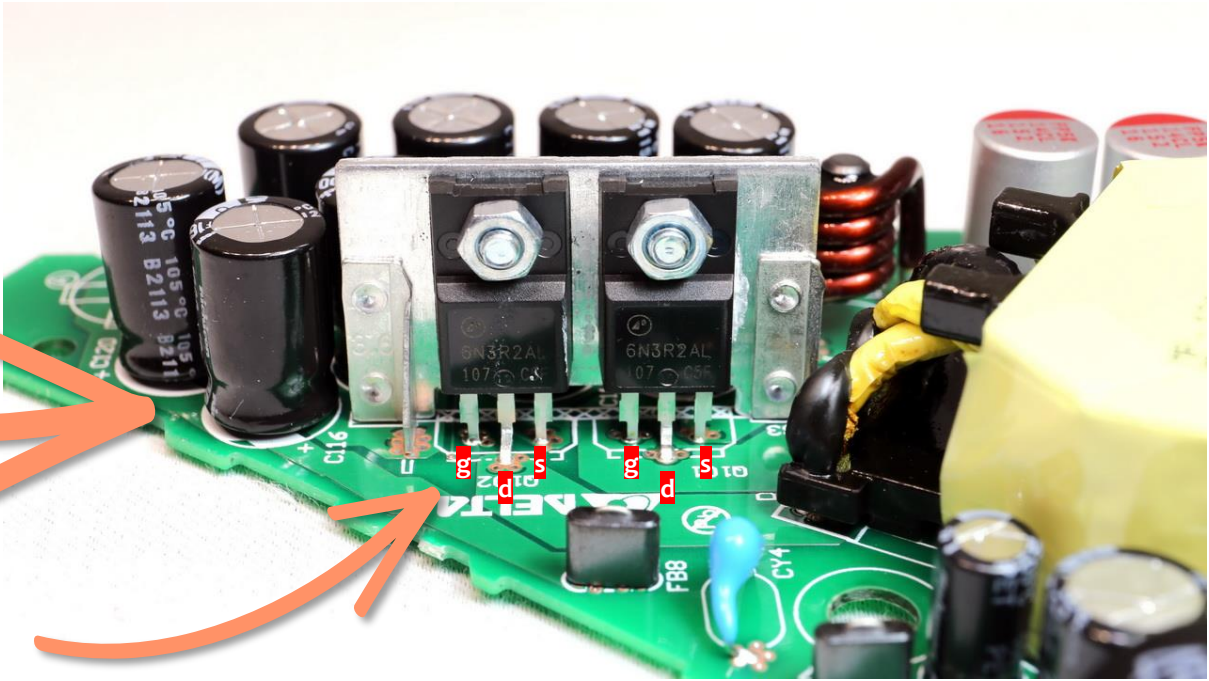Measure output voltage on the secondary filter capacitor



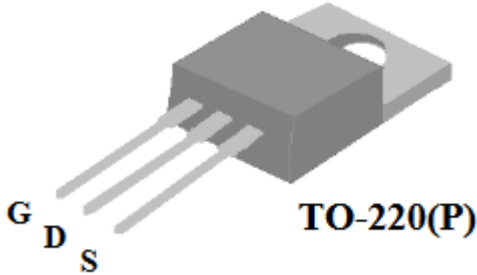PS5 uses fast switching mosfets instead of diodes.



6 common faults with SMPS


5. Power shutdown	Symptom	Cause	Test
When the generated output voltage is too high the SMPS will go in shutdown mode. The SMPS does this too protect the device that is connected to the ouput. In this case the PS5	The rectifier diodes in the secondary section will produce an voltage that goes to +12V and higher to +20V and then to +0V.	-	Multimeter red probe to cold ground. Red probe to the output of the rectifier diode.



Measure output voltage on the secondary filter capacitor



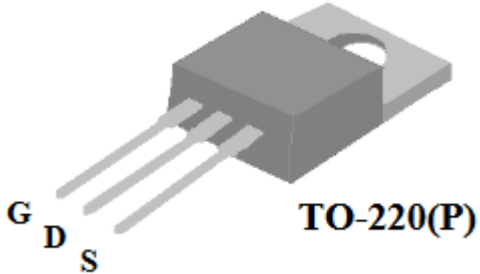PS5 uses fast switching mosfets instead of diodes.




6 common faults with SMPS


6. Intermittent power	Symptom	Cause	Test
The power supply sometimes works ok and sometimes not.	No power Power	Dry solder joint Loose connection Primary side - startup resistor	Visual inspection Measure startup resistor



Front

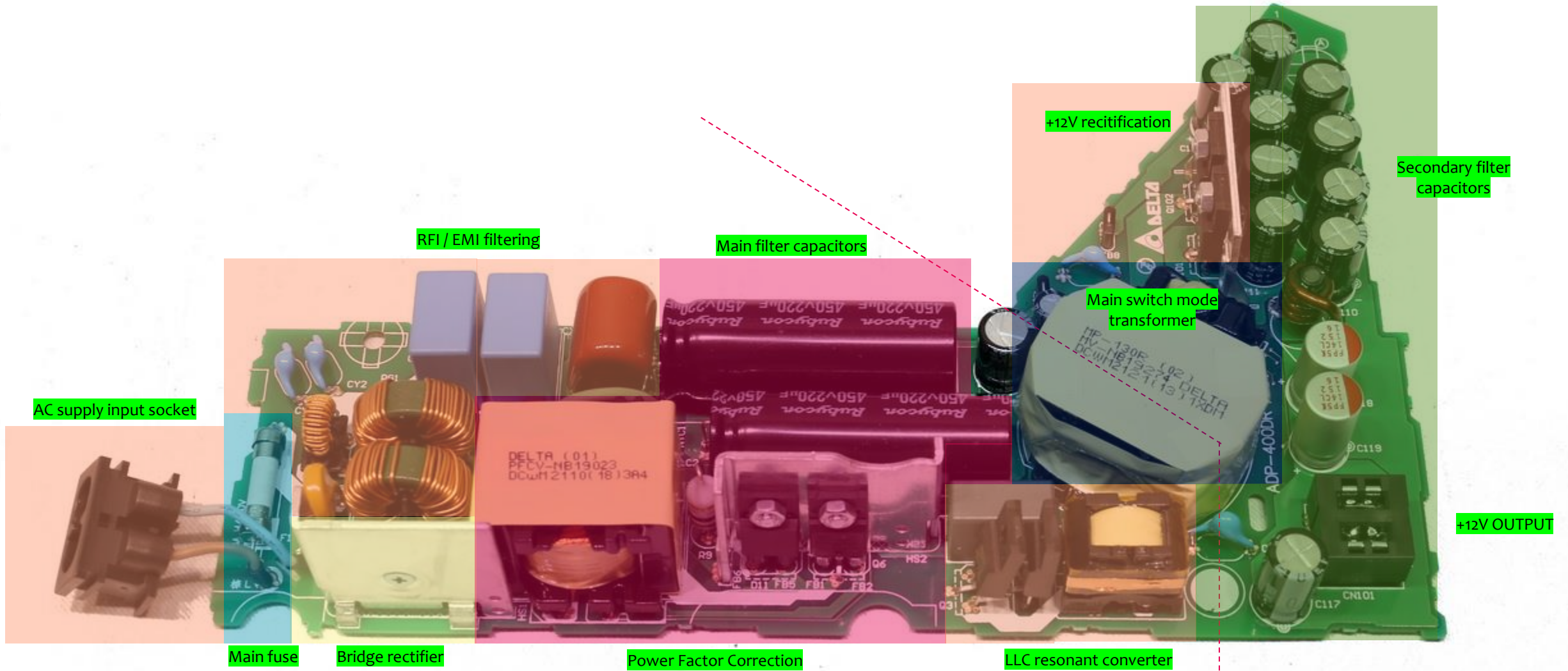

Front

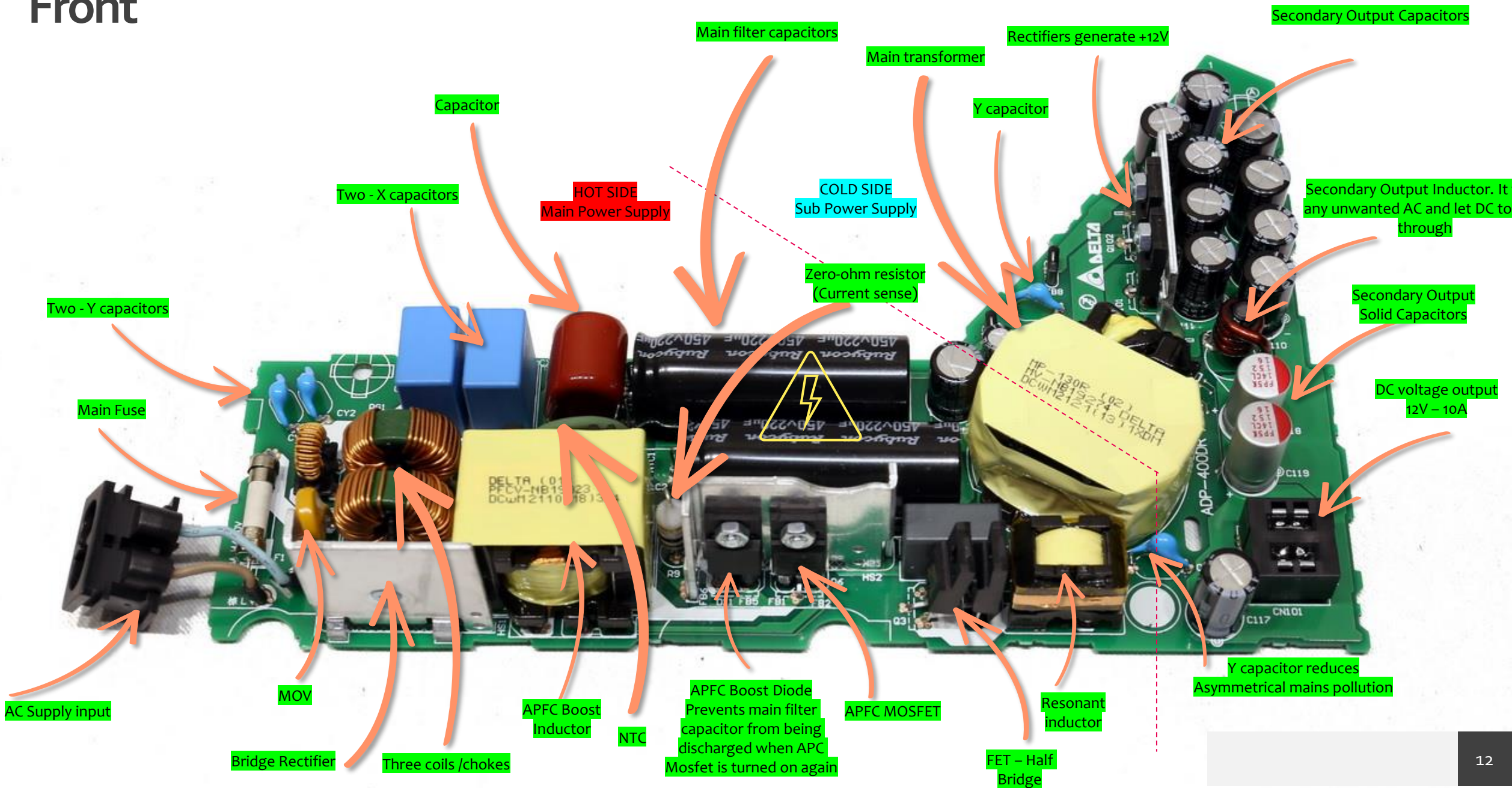

Back


This is a dual
operational
amplifier and
voltage
reference.

Switching Regulator Chip for
synchronous rectification

Optoisolator


APFC / LCC / PWM
Controller

Discharge IC

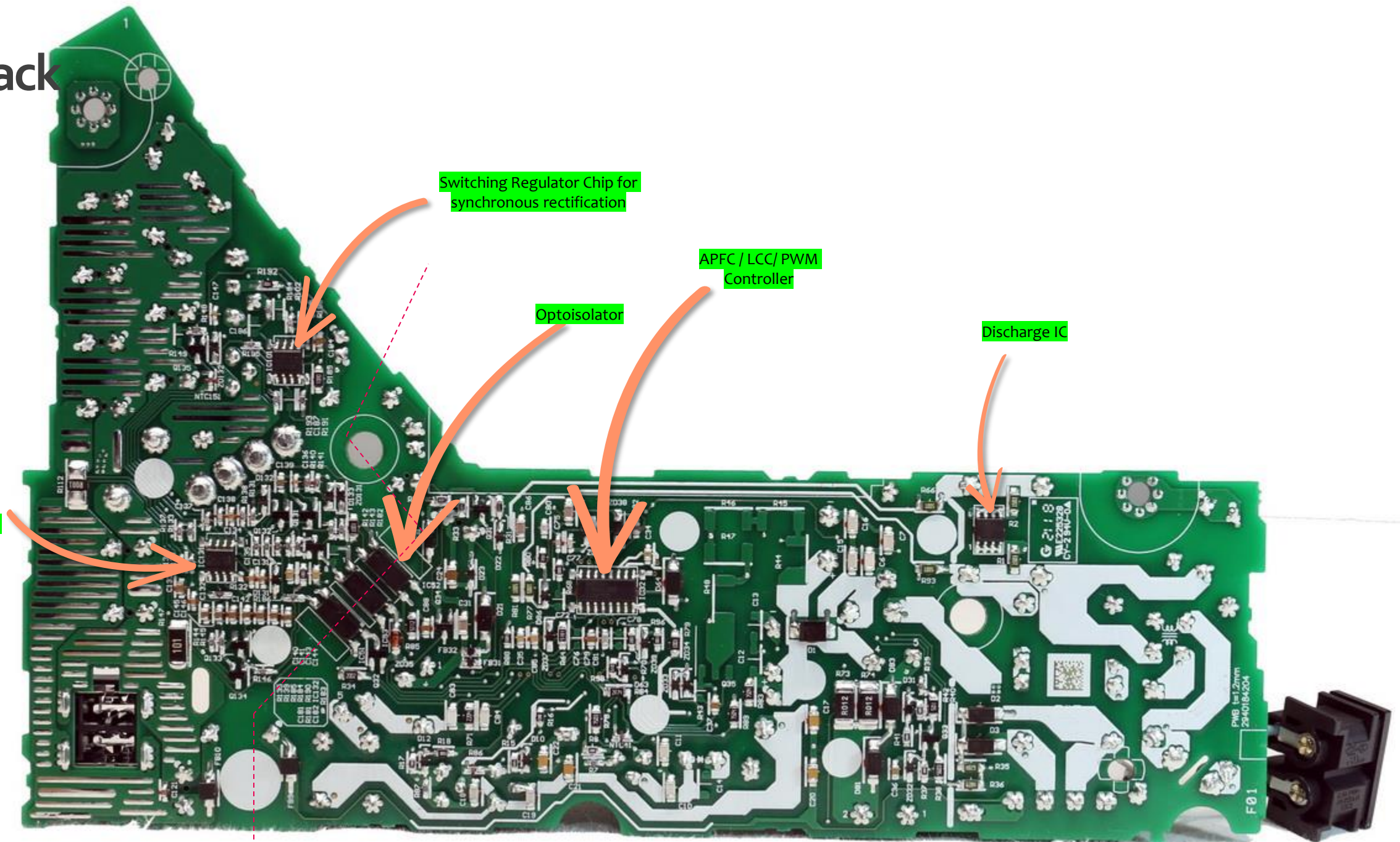

Check inside of case


Search for scorch
marks inside of case

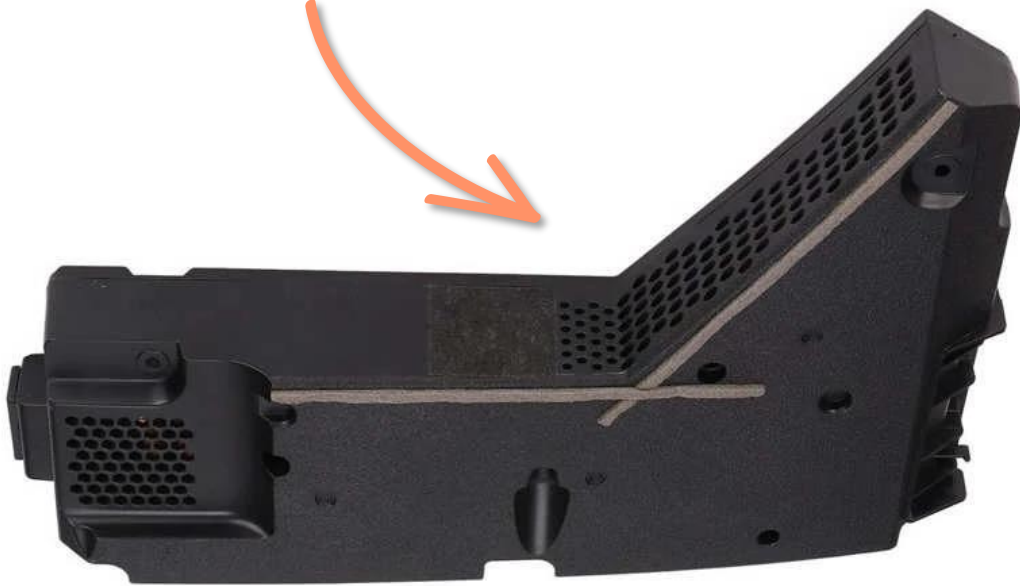


Scorch mark



Voltage Testing – 1.1 AC input voltage


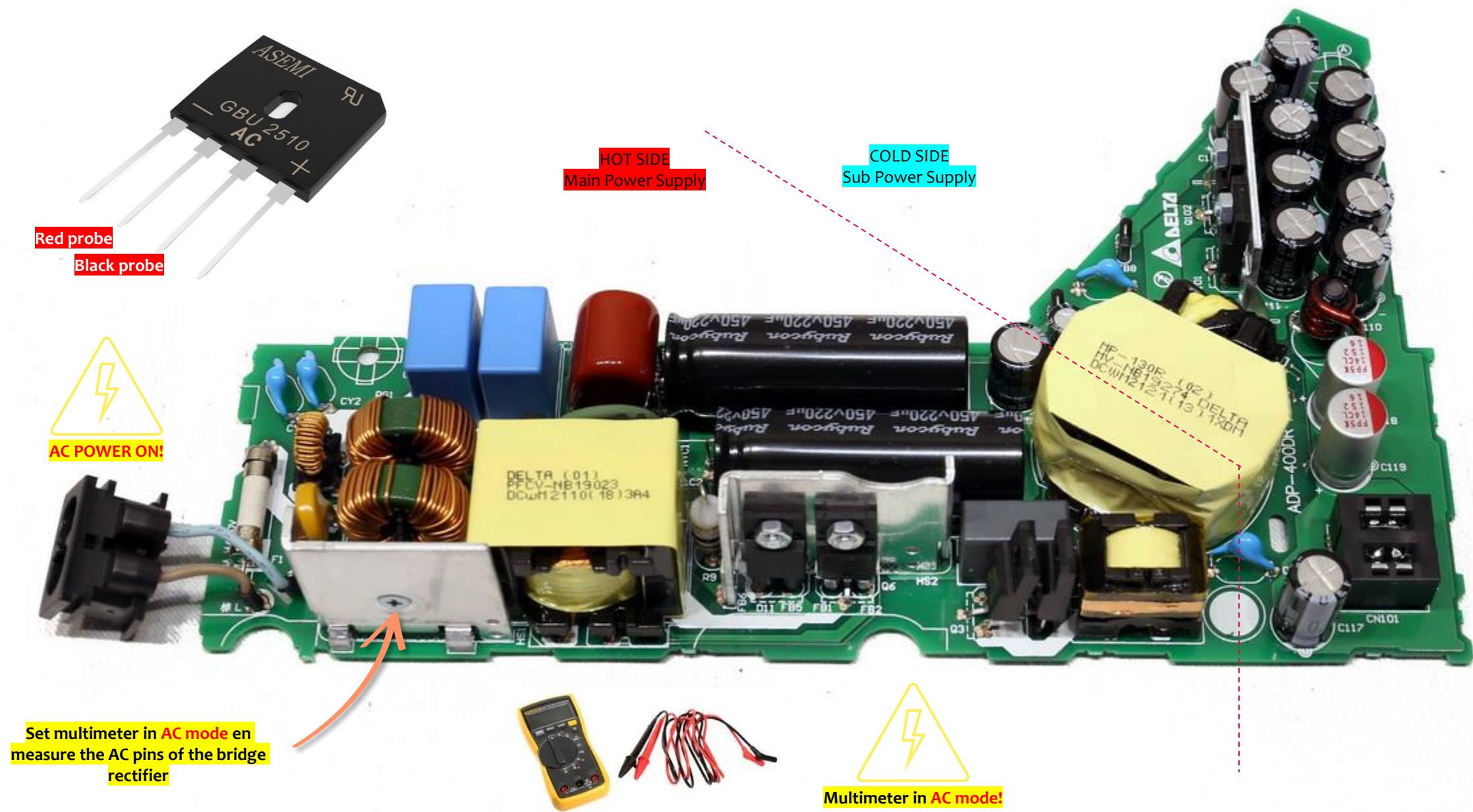


AC POWER OFF!

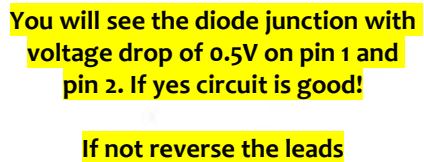

16

Voltage Testing – 1.1.2 AC input voltage

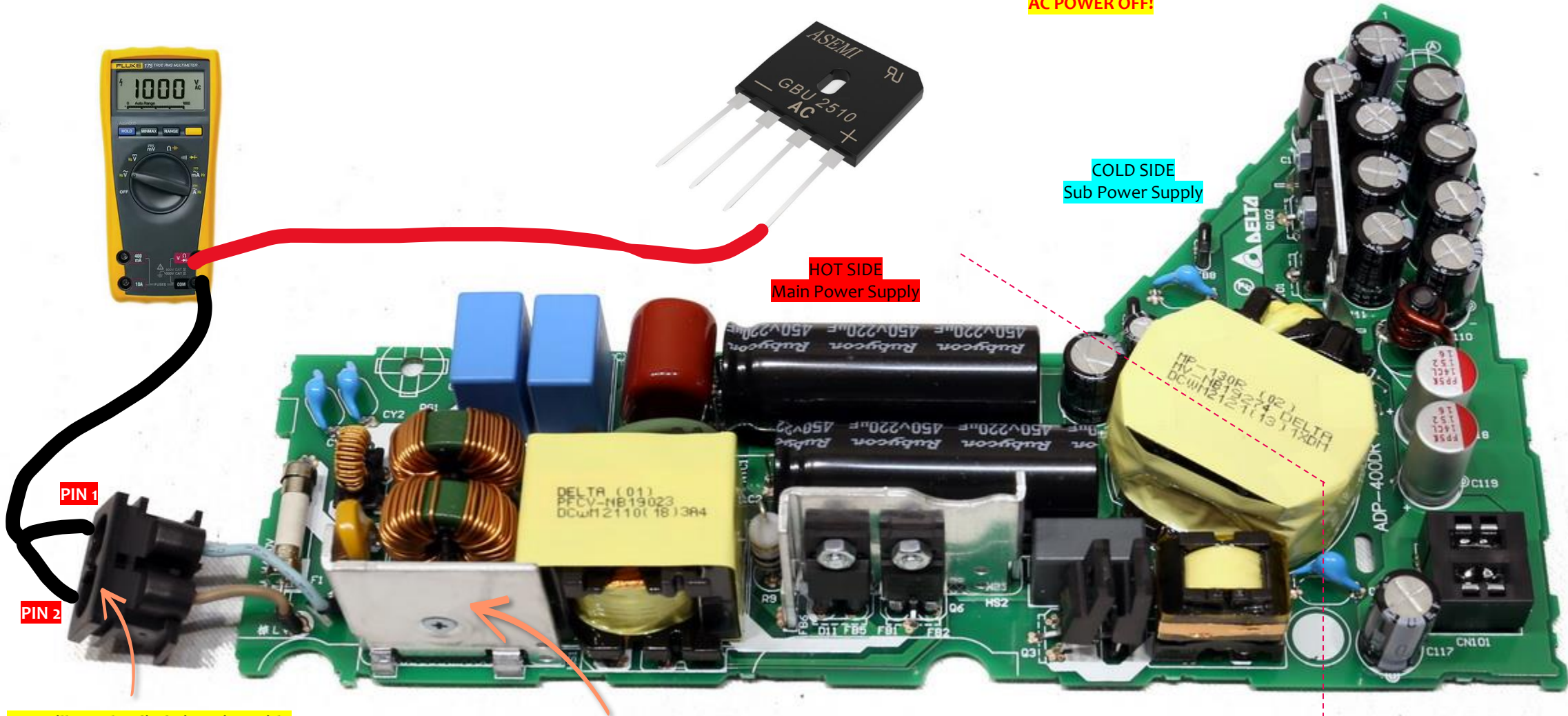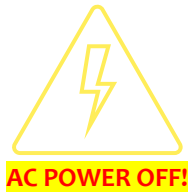

You will see the diode junction with voltage drop of 0.5V on pin 1 and pin 2. If yes circuit is good!

If not reverse the leads

Set multimeter in **DIODE** mode and measure the + and - pins of the bridge rectifier

Voltage Testing – 1.1 AC input voltage

Possible faults

- AC cable unplugged
- AC cable broken
- Main fuse open
- Circuit traces open / dry joint
- EMI coils may have open

Red probe

Black probe

NO VOLTAGE?

Check the components in these area



AC supply input socket

RFI / EMI filtering

Main fuse

Bridge rectifier

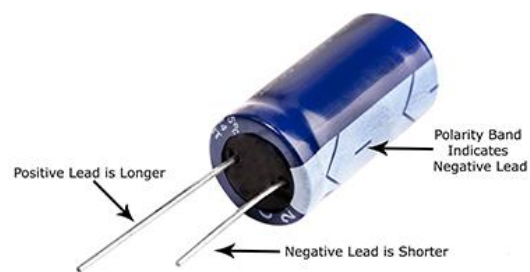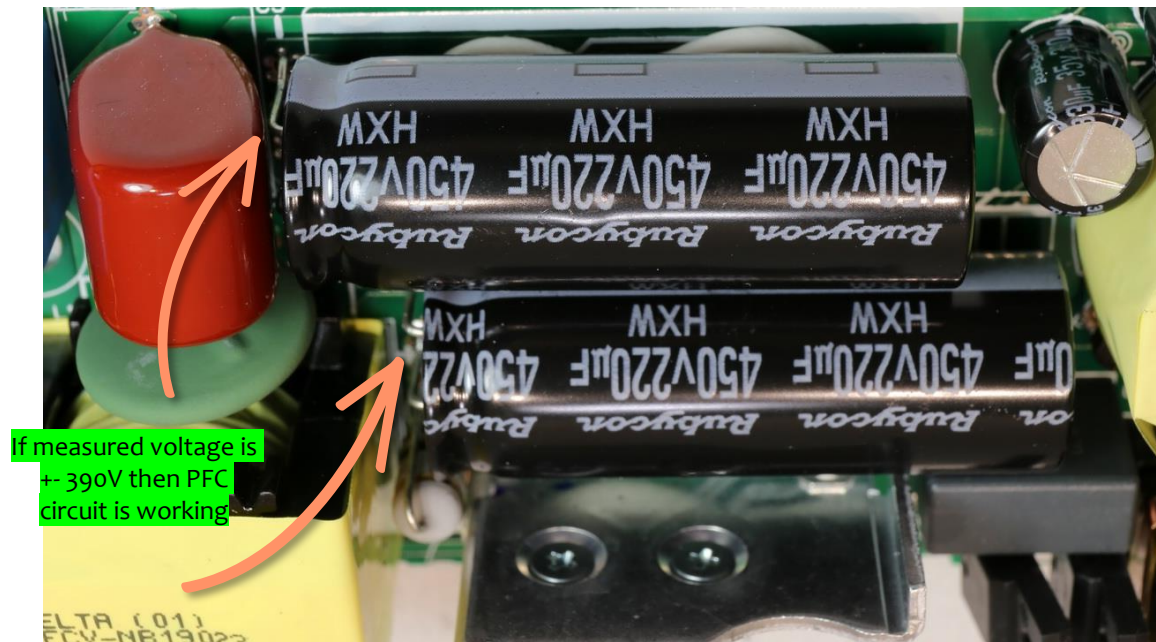Voltage Testing – 1.2 Main filter capacitor



Red probe

Black probe



Multimeter in DC mode!
Don't let the probes touch other pins!



Testing done?
Power off! - discharge capacitor

PFC

Power factor correction (PFC) is a technique used in electrical systems to improve the power factor of an AC power supply. The power factor is a measure of how effectively electrical power is being utilized by a device or system. It represents the ratio of real power (measured in watts) to apparent power (measured in volt-amperes).

< 390V – PFC is not working correctly

> 390V – PFC is not working correctly


0V – Check circuit behind capacitor

Lower voltage than normal check health capacitor with ESR meter

+ 390V – PFC is ok when a load is connected to the 12V output of 8 – 10 amps

+ 380V – PFC is ok when NO load is connected to the 12V output

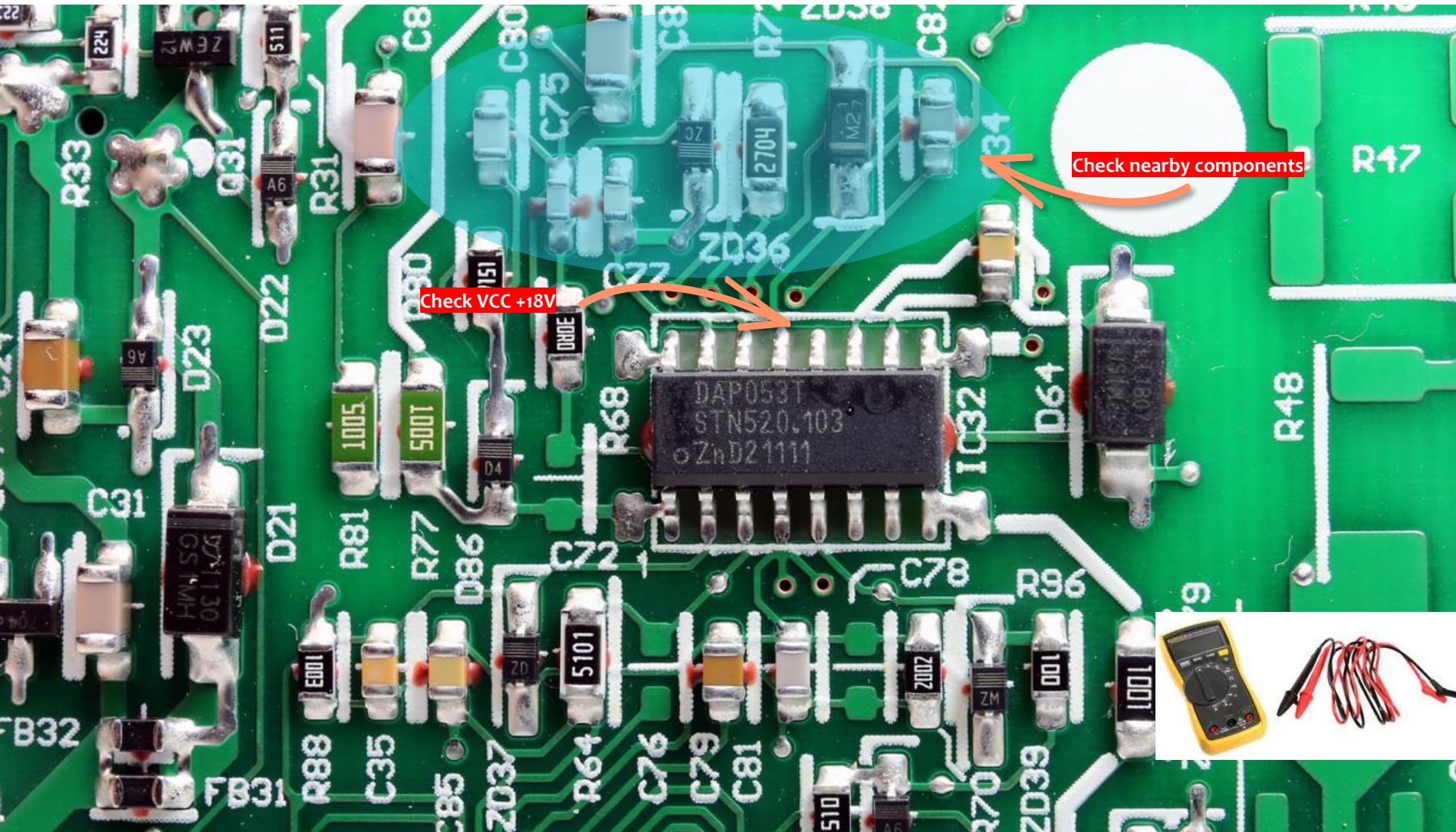Voltage Testing – 1.3 Supply voltage VCC – PWM IC



VCC - PIN

Identify the VCC Pin of the PWM / Power IC: Look at the datasheet or pinout diagram of the specific PWM power IC you are using. The VCC pin is usually marked clearly in the documentation.

For PS5 it is **+18V**.

VCC is needed to power the PWM / Power IC on to generate the voltages.

Correct voltage is present. We can assume now the filter capacitor; startup resistor and bridge rectifier are ok.

0V - and main filter capacitor has the correct voltage then the startup resistor could be shorted pulling the VCC down to 0V.

Voltage lower than expected and main filter capacitor has the correct voltage then the resistance of startup resistor could be high ohm. Or components nearby are leaky or faulty




AC POWER ON!

Voltage Testing – 1.4 Secondary Output Voltages



Check output voltage

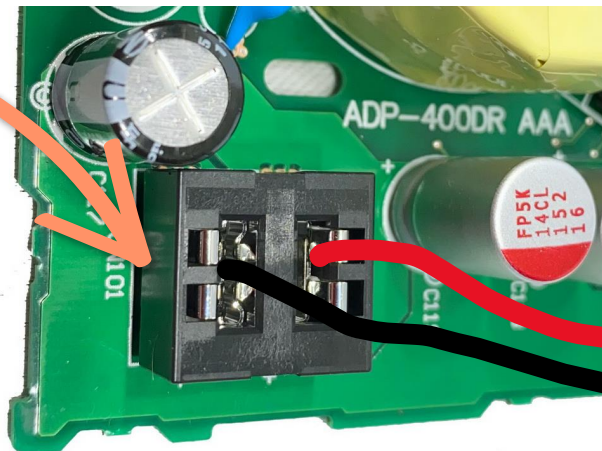

To test output voltage, you need to connect an electronic load. For PS5 it is +12V and 8 Amp of current



Testing output voltages on the cold side you need to know what voltages are generated.

For PS5 it is 12V / 10 amp

Some SMPS have multiple outputs with different voltages.

Output voltage is OK, no action needed.

0V - SMPS is faulty or some short is preventing the SMPS from starting

Low output voltages then specified. Problem could be on the hot or cold side. Current sense resistor could have a different value or one of the secondary filter capacitor has a high ESR.

Higher output voltage. If it is too high the SMPS will shutdown. When slightly high the problem could be in the feedback circuit area, a resistor or optoislator turned into high ohm.


Output is power cycling. Max voltage to zero voltage and then it repeats. Cause can be in hot or cold side.

SMPS shutdown. You will see that the output voltage goes up and then down. When you switch the SMPS off and on the same thing happens.


Voltage Testing – 2.1 Use oscilloscope to test waveforms



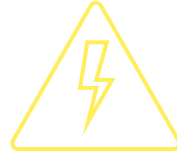Use the Isolator transformer
When you are measuring the hot side
with a oscilloscope!



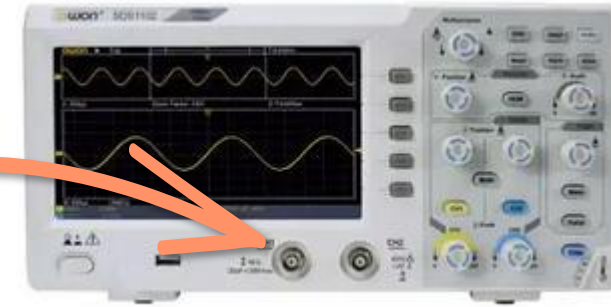**DO NOT TOUCH THE ROUND METAL
CONNECTORS!**



HOT SIDE
Main Power Supply


Test PWM signal of
power IC on the HOT
side

COLD SIDE
Sub Power Supply

Test waveform on the
DC output of the cold
side at the output of
the diodes.

In PS5 this would be
testing the MOSFET's
and IC that drives the
mosfets and the
output line.

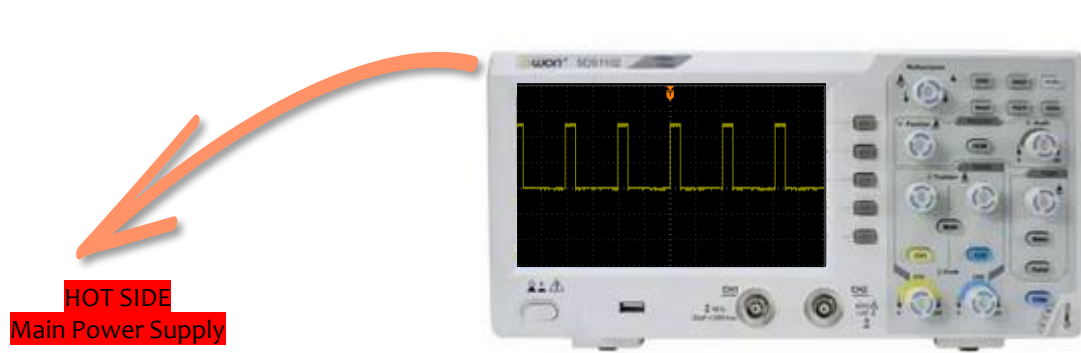
Voltage Testing – 2.1 Use oscilloscope to test PWM waveforms



Test PWM signal on
the gate output of
high and low side
mosfet



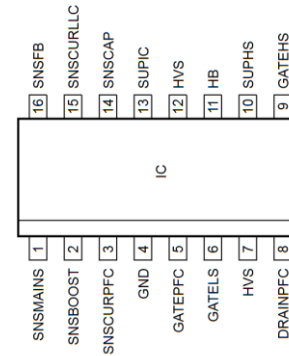i
Set oscilloscope
in AC mode
Set the time and voltage



Gate high side mosfet




Gate low side mosfet


Good output signal means: IC is getting power,
components near the IC are working.
Troubleshoot the cold side.

No output signal but the IC is getting
correct power then: IC could be faulty,
Mosfet is shorted, Primary winding of
main transformer is shorted or a short
on the cold side.

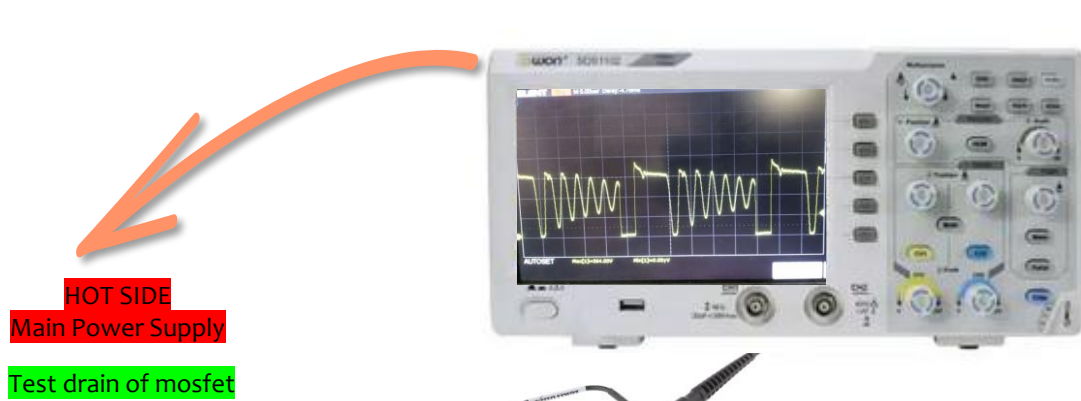
Voltage Testing – 2.2 Use oscilloscope to test drain of mosfet



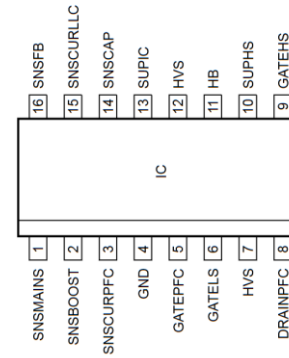
i
Set oscilloscope
in AC mode
Set the time and voltage



See the signal of the drain pin.

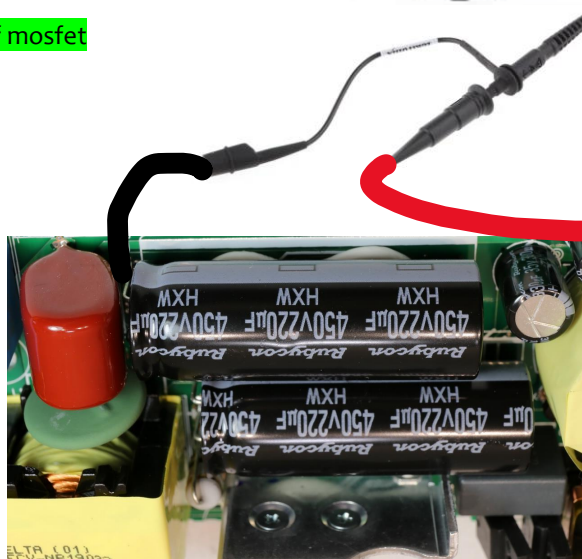

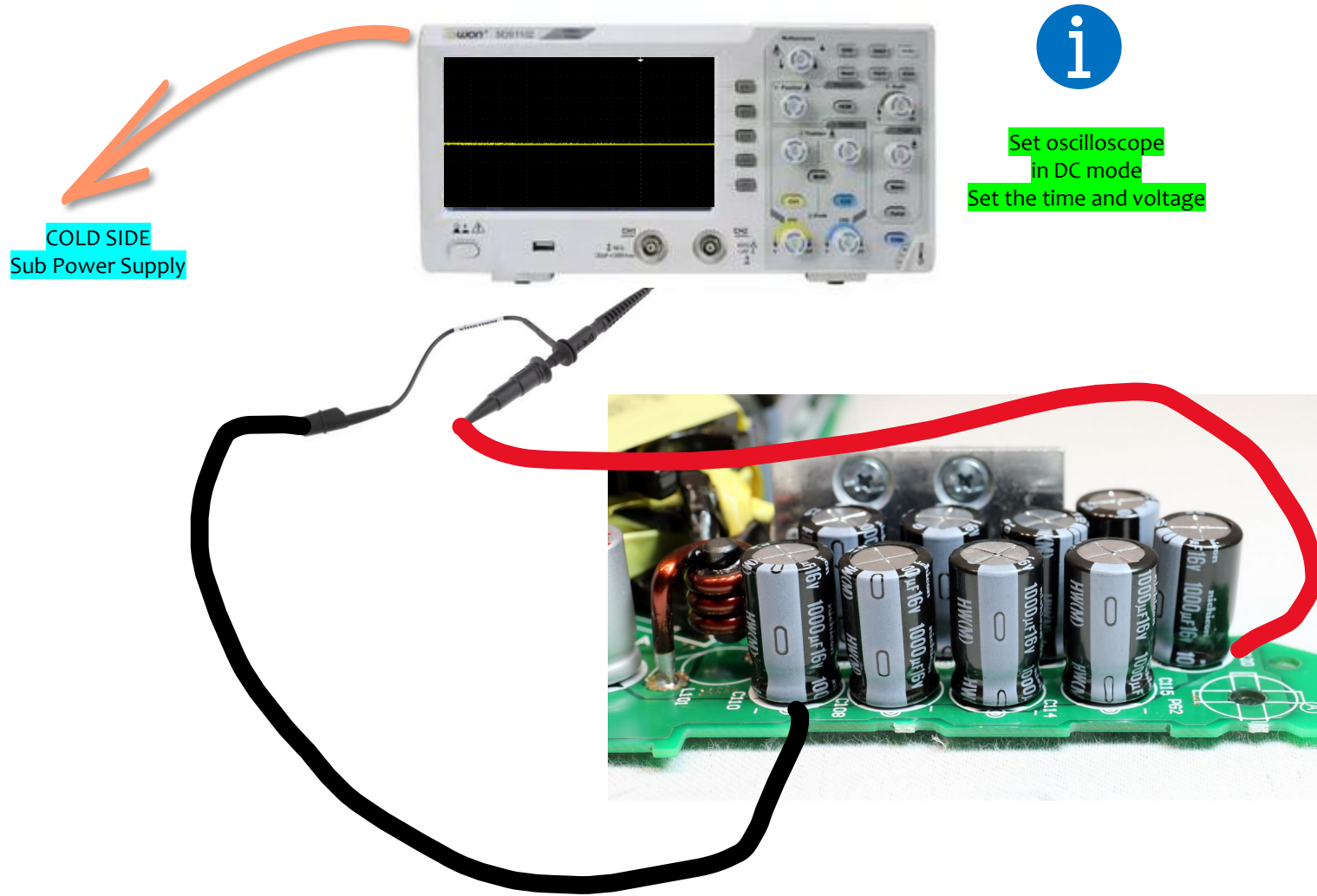
Voltage Testing – 2.2 Use oscilloscope to test DC output voltage




The DC output voltage generated should be a clean DC voltage. On the scope the waveform should be a straight horizontal line without distortion and ripples.

When the DC output voltage is clean you can assume the main and secondary filter capacitors are working ok.

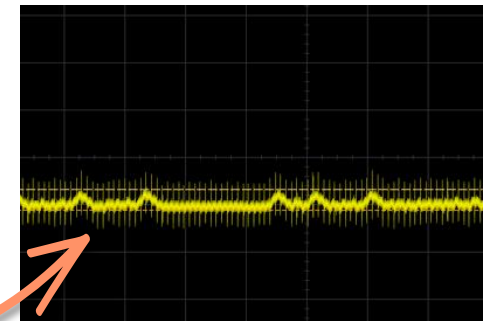When the DC output voltage has ripple you need to check all the filter capacitors with a ESR meter.



Troubleshooting – Bridge rectifier

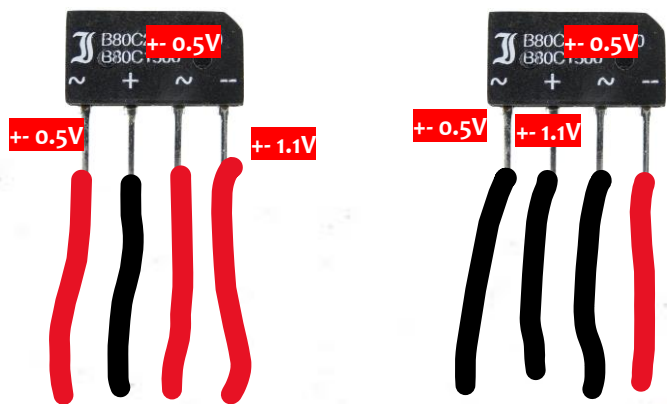


Main fuse is open

Shorted rectifier

HOT SIDE
Main Power Supply

COLD SIDE
Sub Power Supply

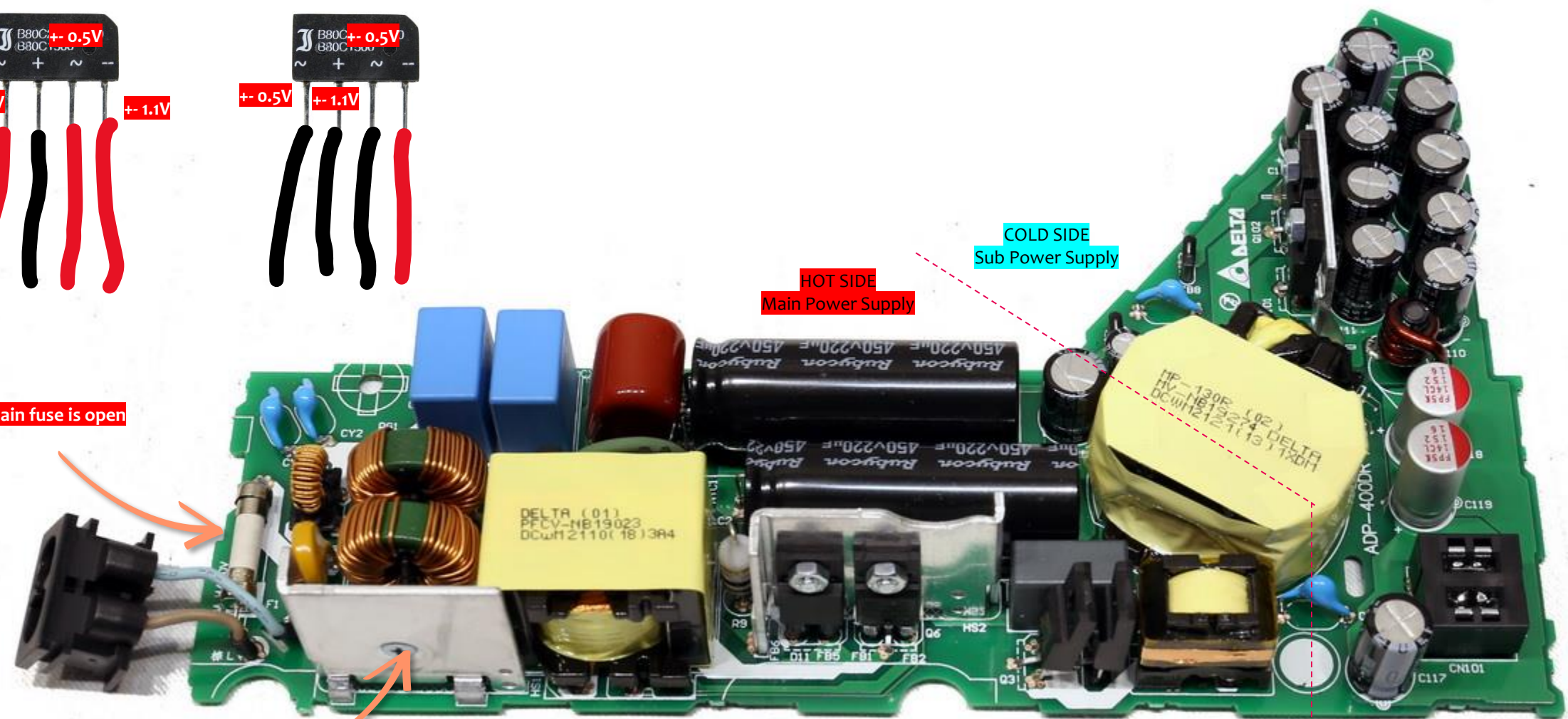

Troubleshooting – Main filtering capacitor


Filter capacitor

- Value drops
- Open circuit
- ESR value is high
- Bulged
- Short circuit
- Breakdown under load


HOT SIDE
Main Power Supply

COLD SIDE
Sub Power Supply

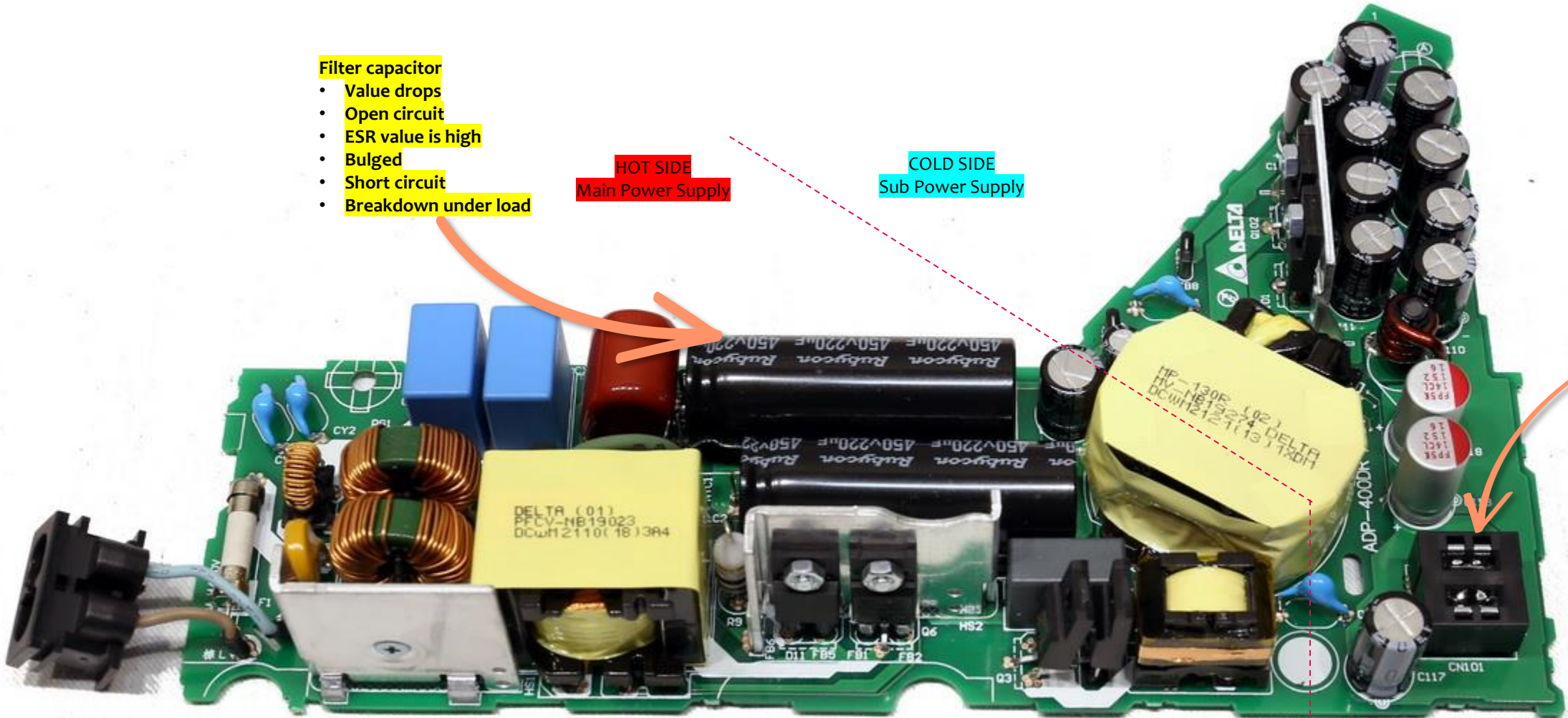- No voltage
- Voltage blink
- Unstable voltage



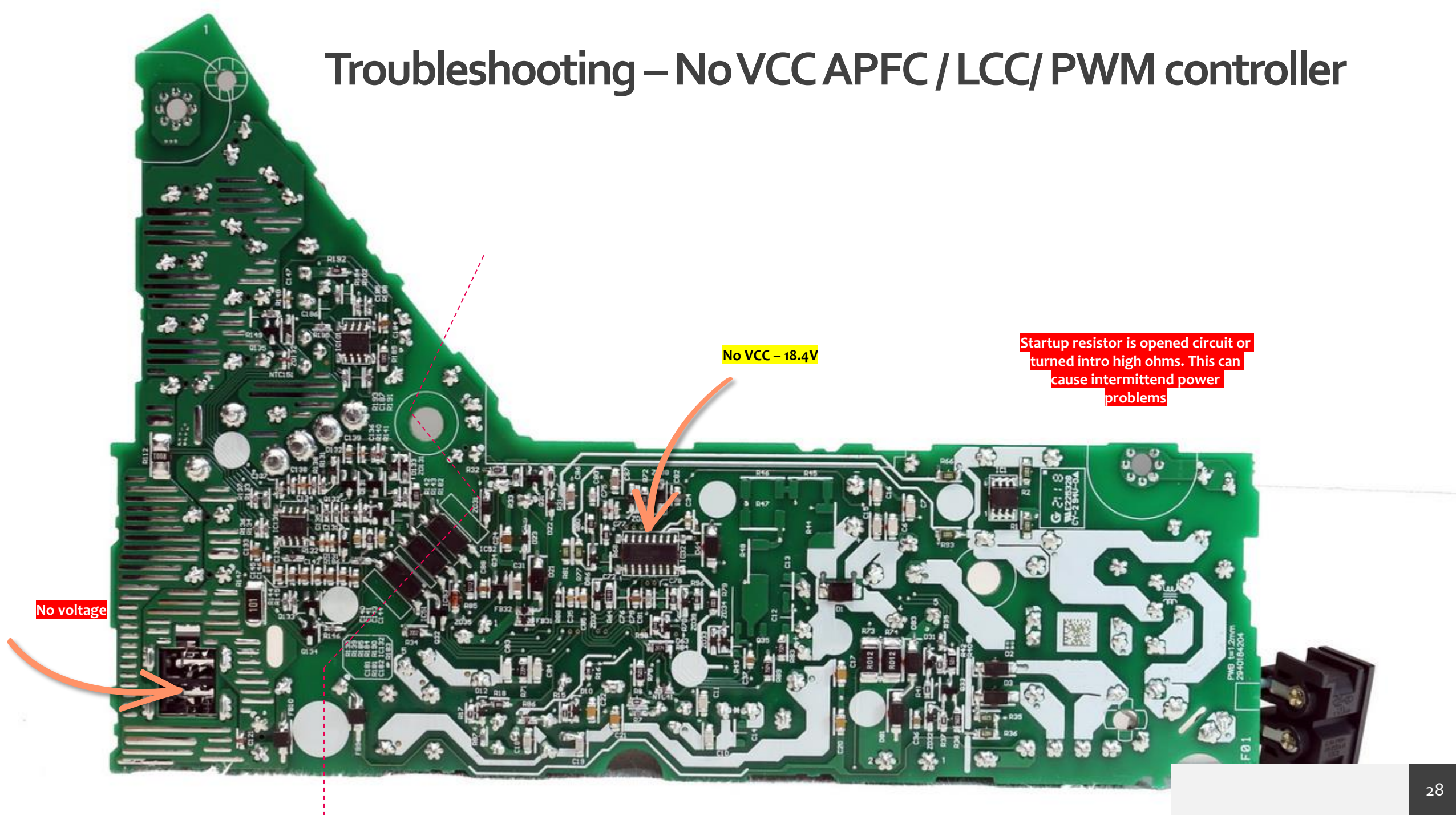Troubleshooting – No VCC APFC / LCC / PWM controller



Troubleshooting – Optoisolator

If the optoisolator is faulty, like open LED, leaky or shorted

Regulation circuit

voltage er supply is on

If the optoisolator is faulty, like open LED, leaky or shorted



Regulation circuit

- Voltage blink
- Lower output voltage
- Shutdown after supply is on


APFC / PWM controller IC

DAP053T

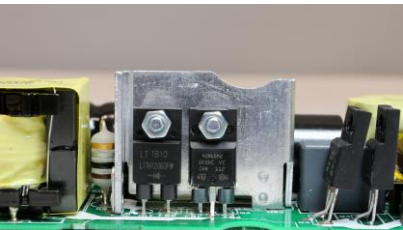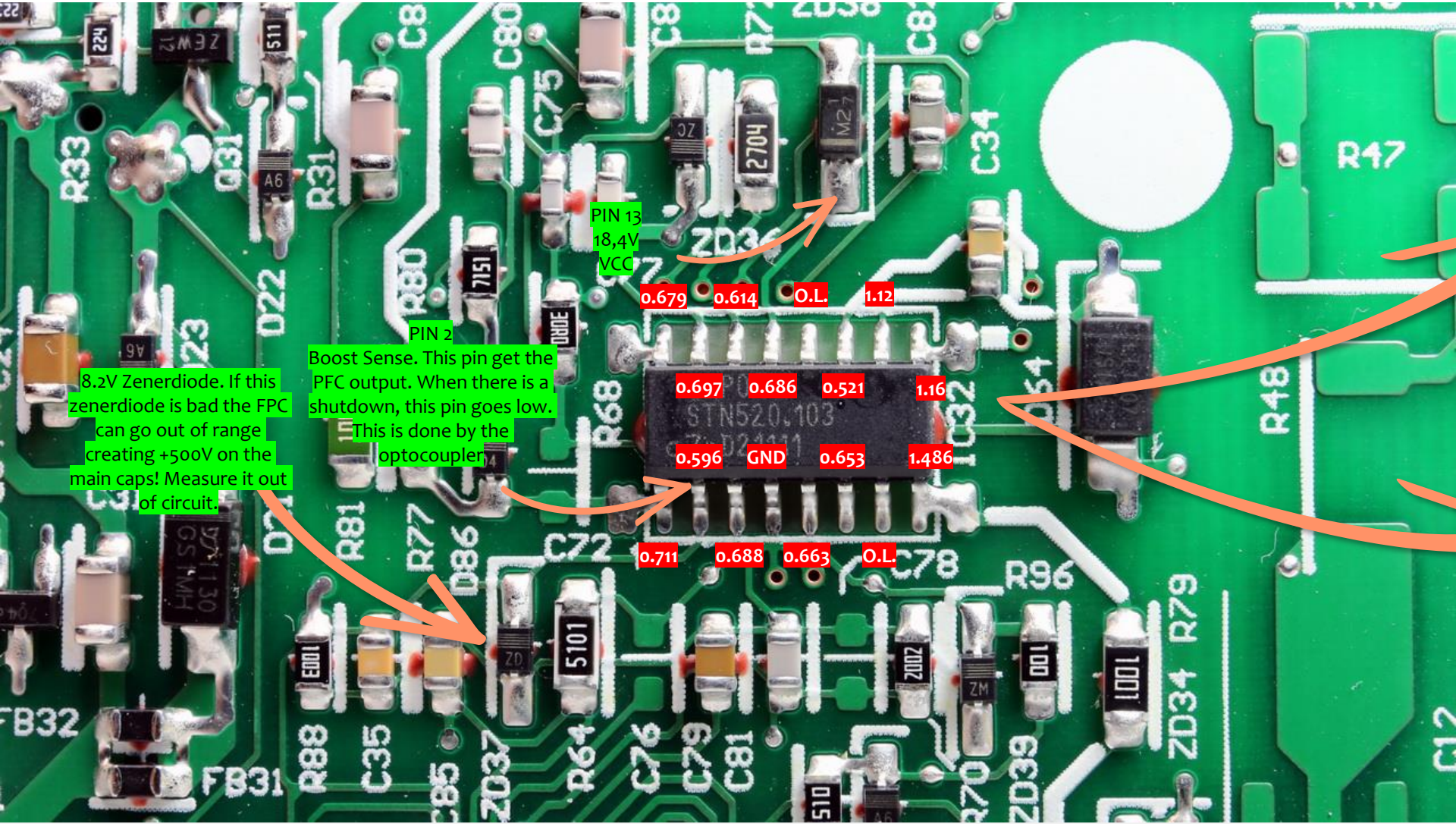Measure IC for shorts and measure each pin in diode mode using the multimeter



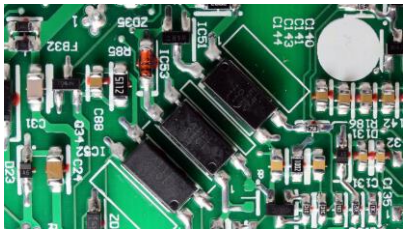APFC Boost Diode
APFC MOSFET
LLC High and Low side mosfet




Powergood
Feedback
Shutdown

= diode measurements

APFC / PWM controller IC

DAP053T = TEA2016AAT

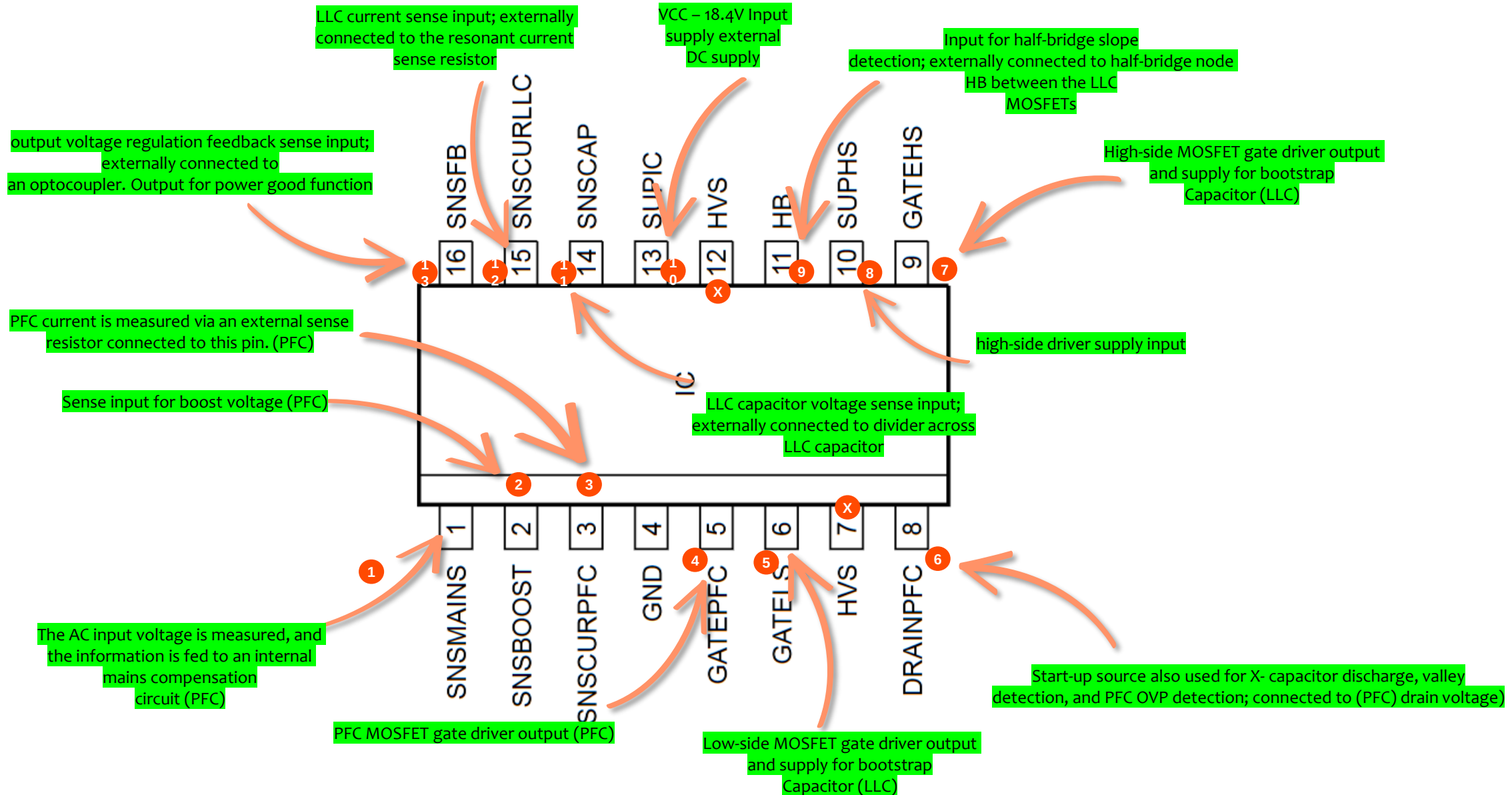



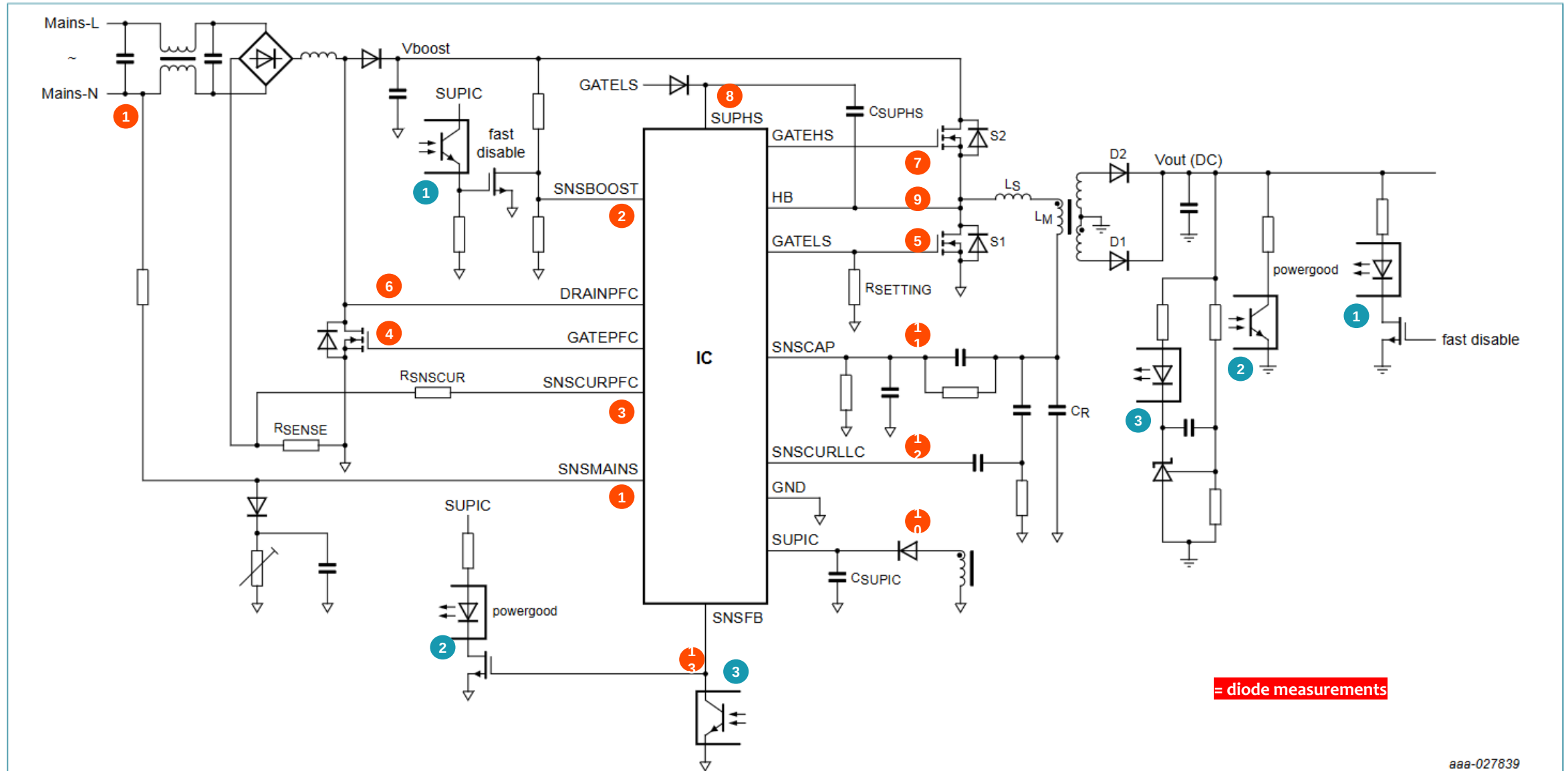


Figure 25. TEA2016AAT application diagram

Front

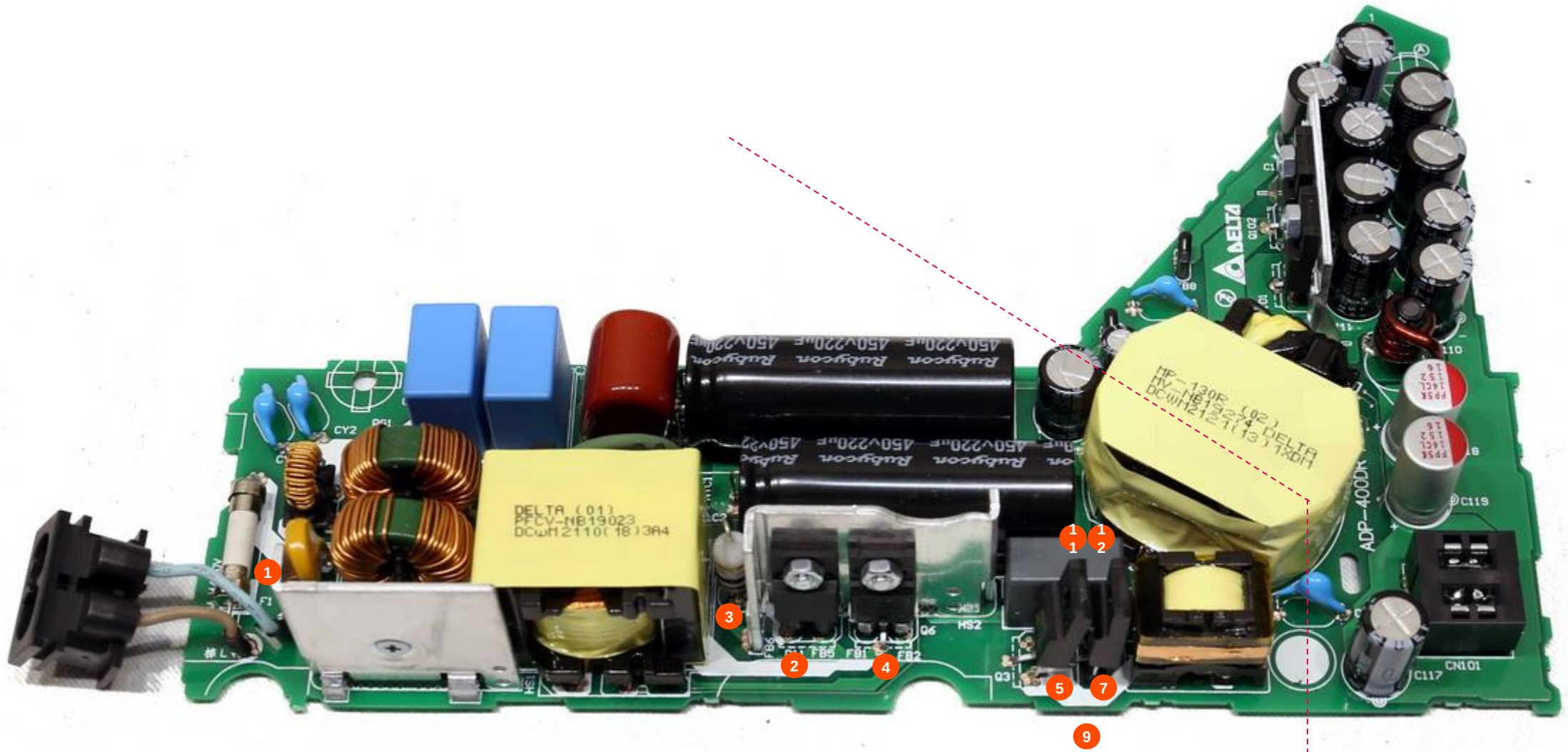


APFC / PWM controller IC

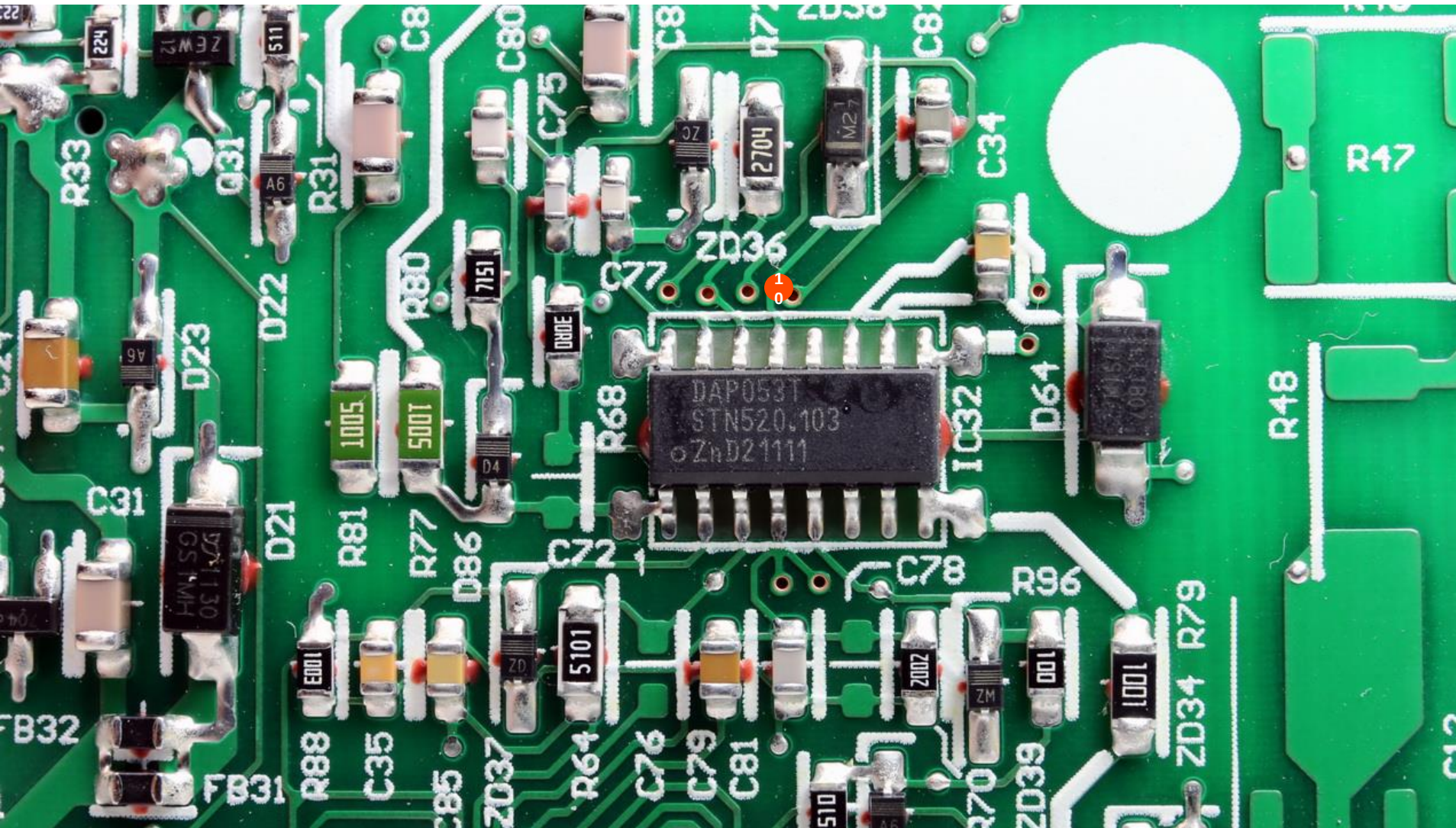

Synchronous rectification


MP6924A

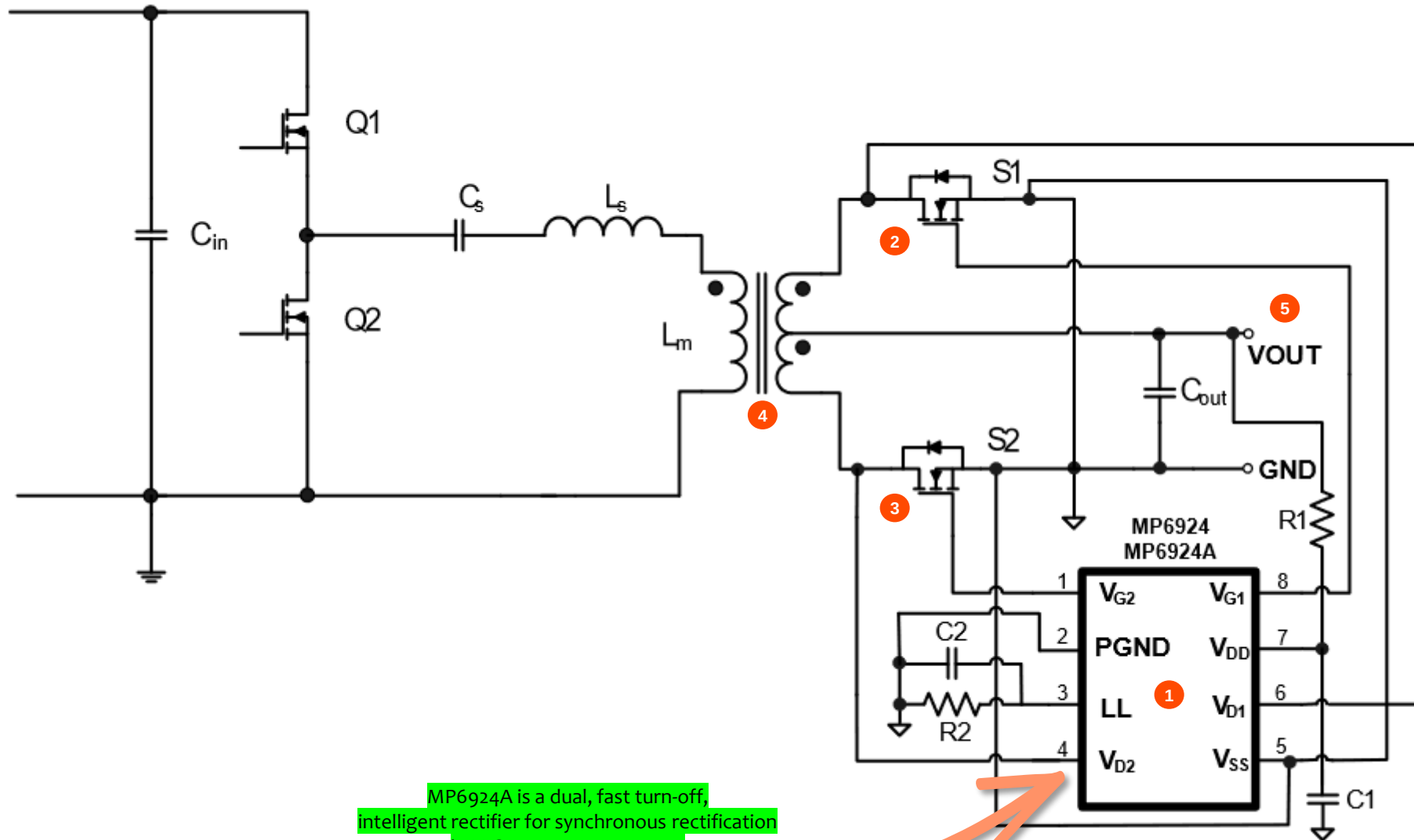

MP6924A is a dual, fast turn-off, intelligent rectifier for synchronous rectification in LLC resonant converters

Synchronous rectification

MP6924A

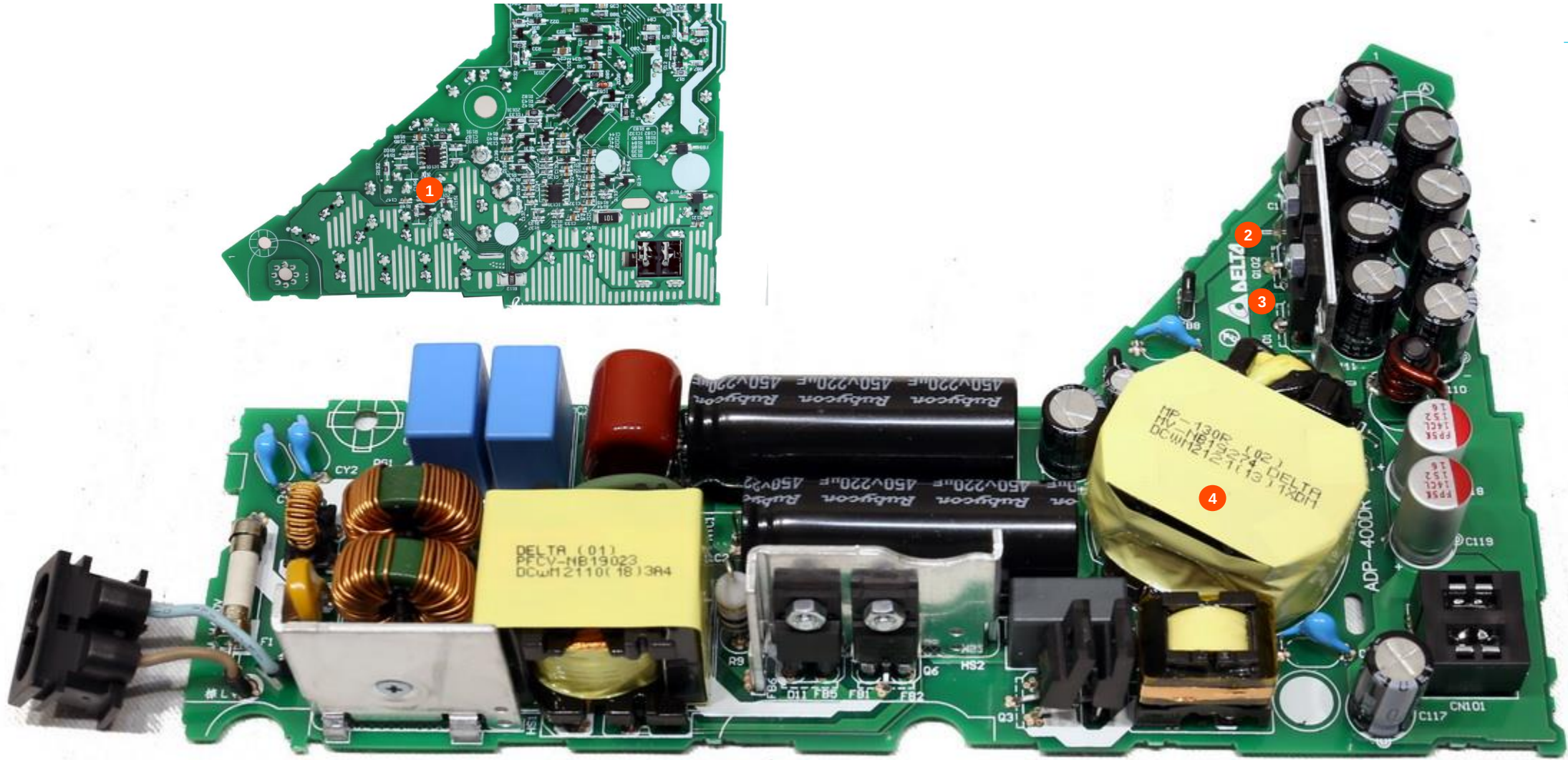

Power supply failing under load


Conditions

The PS5 power supply can deliver more than 30 Amps and 12V.

If the electronic load is connected set the voltage to 12V and then increase load current in intervals of 1 Amp.

The voltage of 12V must not drop when you increase the load current until 10 amps.

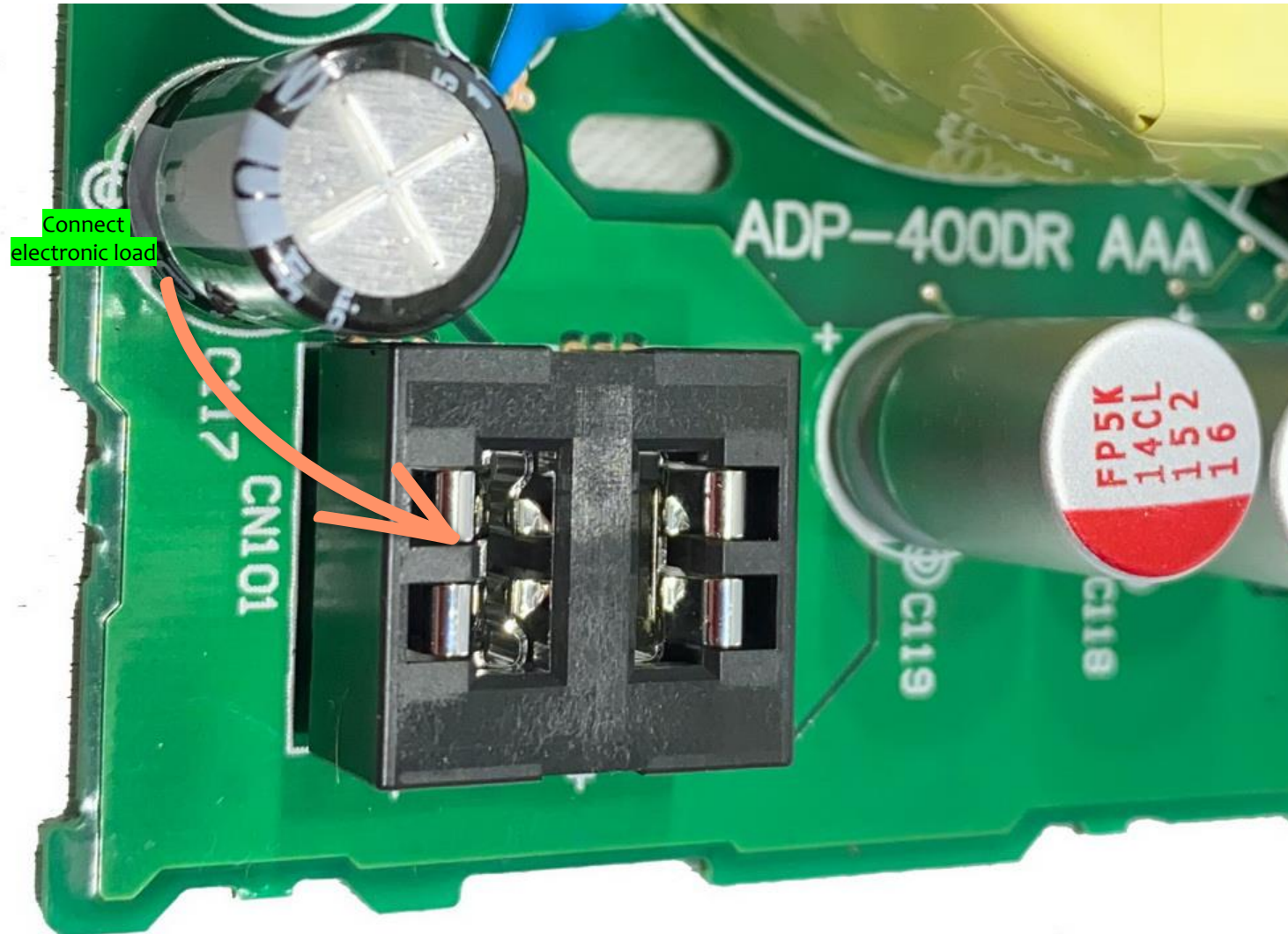When the voltage is dropping below 12V when you increase the current the power supply is failing under load.



Measure main filter capacitor under load and no load.

With load connected: 390V
No load connected: 385V

Measure APFC / PWM controller IC in diode mode for deviations in value.

To eliminate that the shutdown circuit is causing the problem disable the transistor that is connected to pin 2. If the main capacitor is still too low then replace the APFC / PWM IC.



Electronic load results

Working APFC

Load voltage (v)	Load current (A)	Main filter capacitor (v)
+12V	4	+ - 390
+12V	5	+ - 390
+11.9V	6	+ - 390
+11.9V	7	+ - 390
+11.9V	8	+ - 390
+11.8V	9	+ - 390
+11.8V	10	+ - 390

Not correctly working APFC


Load voltage	Load current (A)	Main filter capacitor (v)
+12V	4	+ - 390
+12V	5	+ - 390
+11.8V	6	+ - 385
+11.7V	7	+ - 360
+11.7V	8	+ - 360
+11.6V	9	+ - 350
+11.6V	10	+ - 330

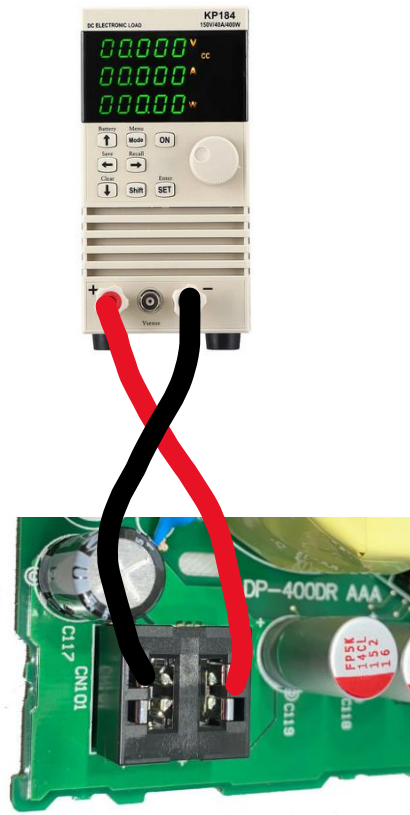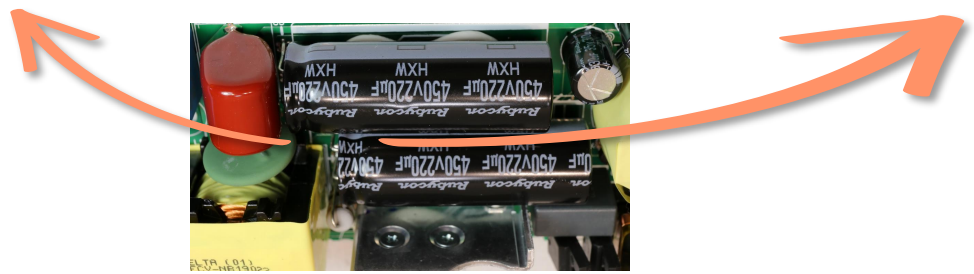


Fast shutdown on output

Shutdown symptoms

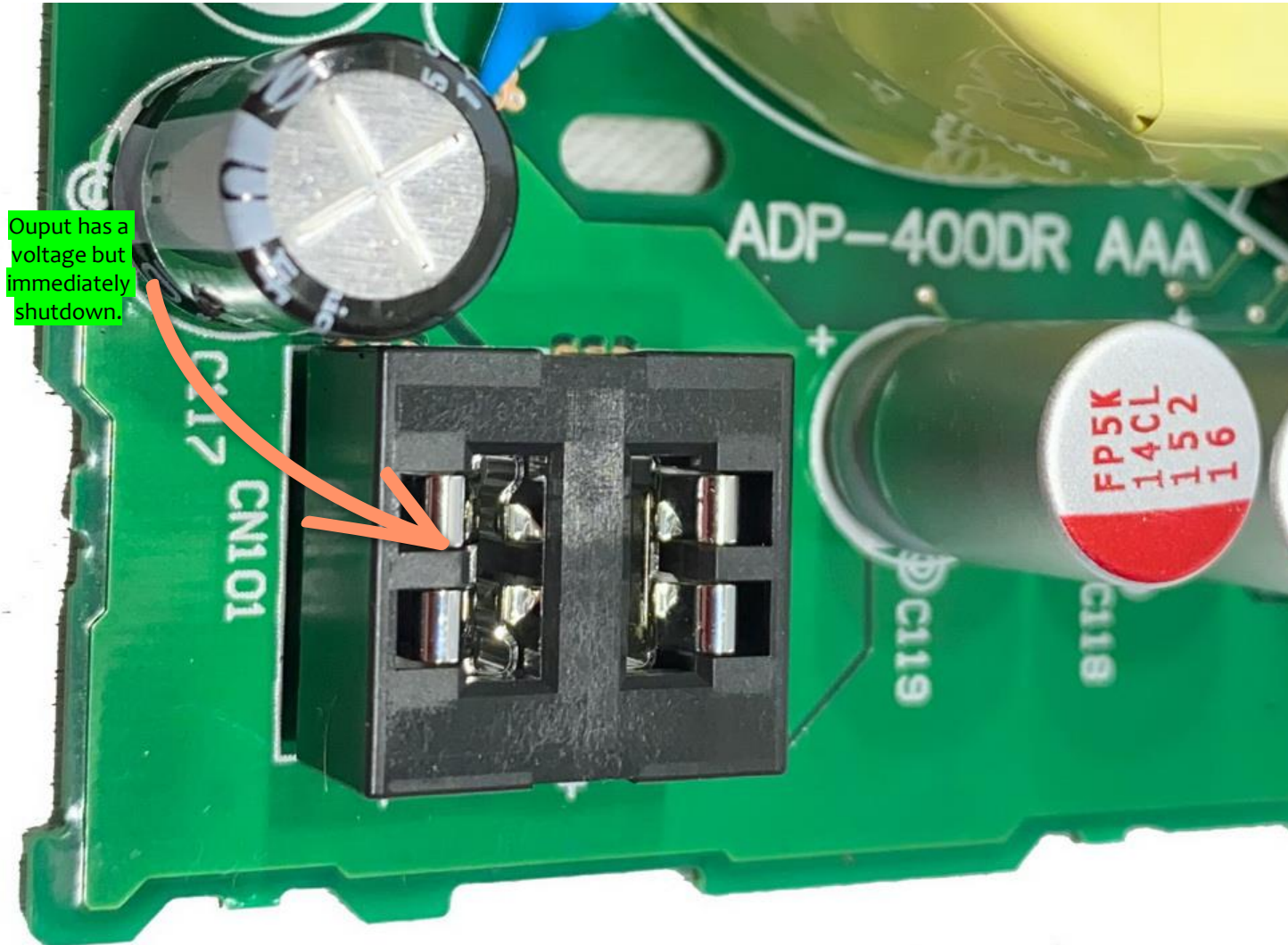If you see a voltage being created on the output but then it goes to 0. This means that the power supply wants to generate the voltage, but something is triggering a shutdown.



Measure output for shorts

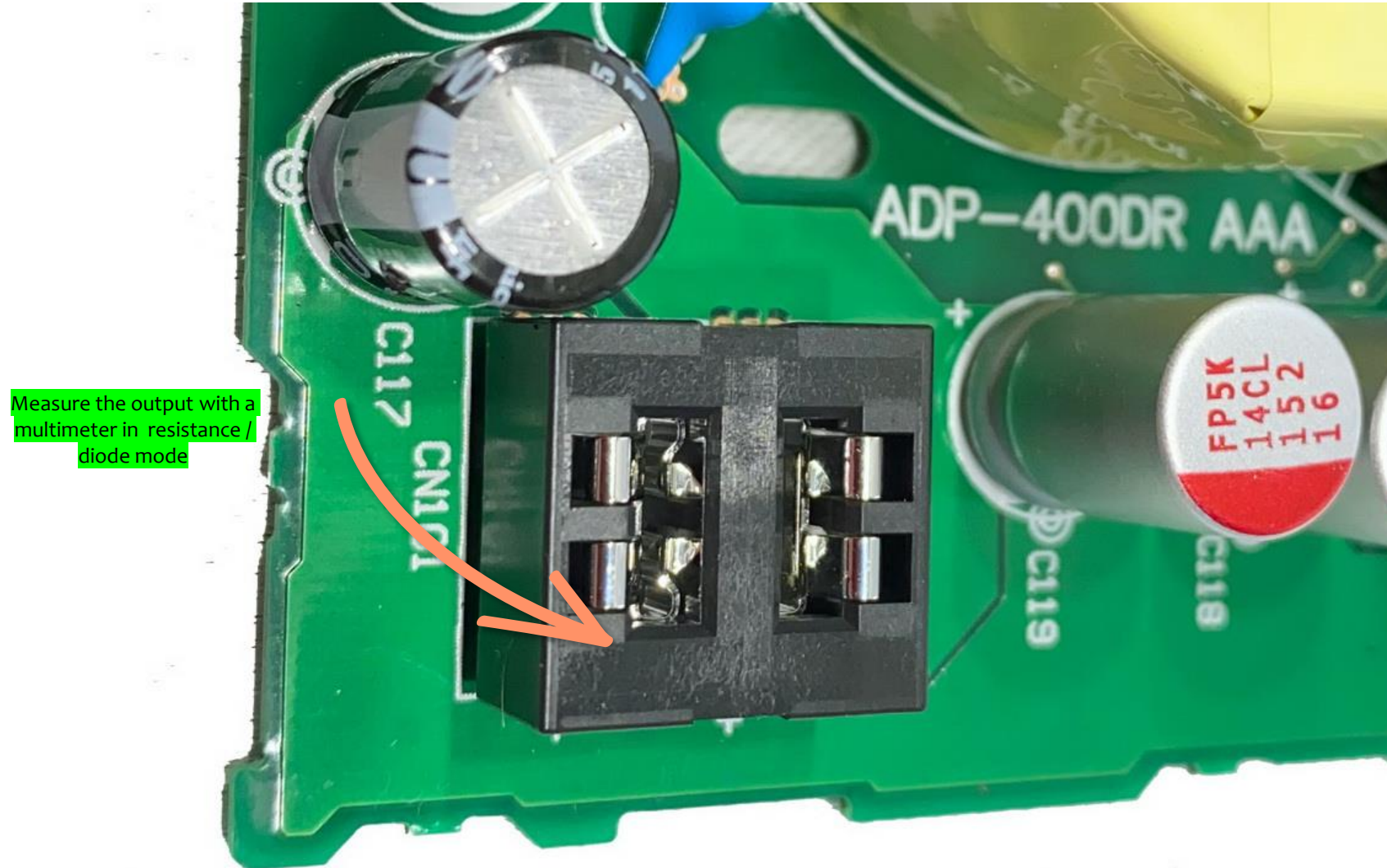


If there is a short on the cold / secondary side. Check all capacitors and rectifier diodes

+12V Output shorted – possible causes



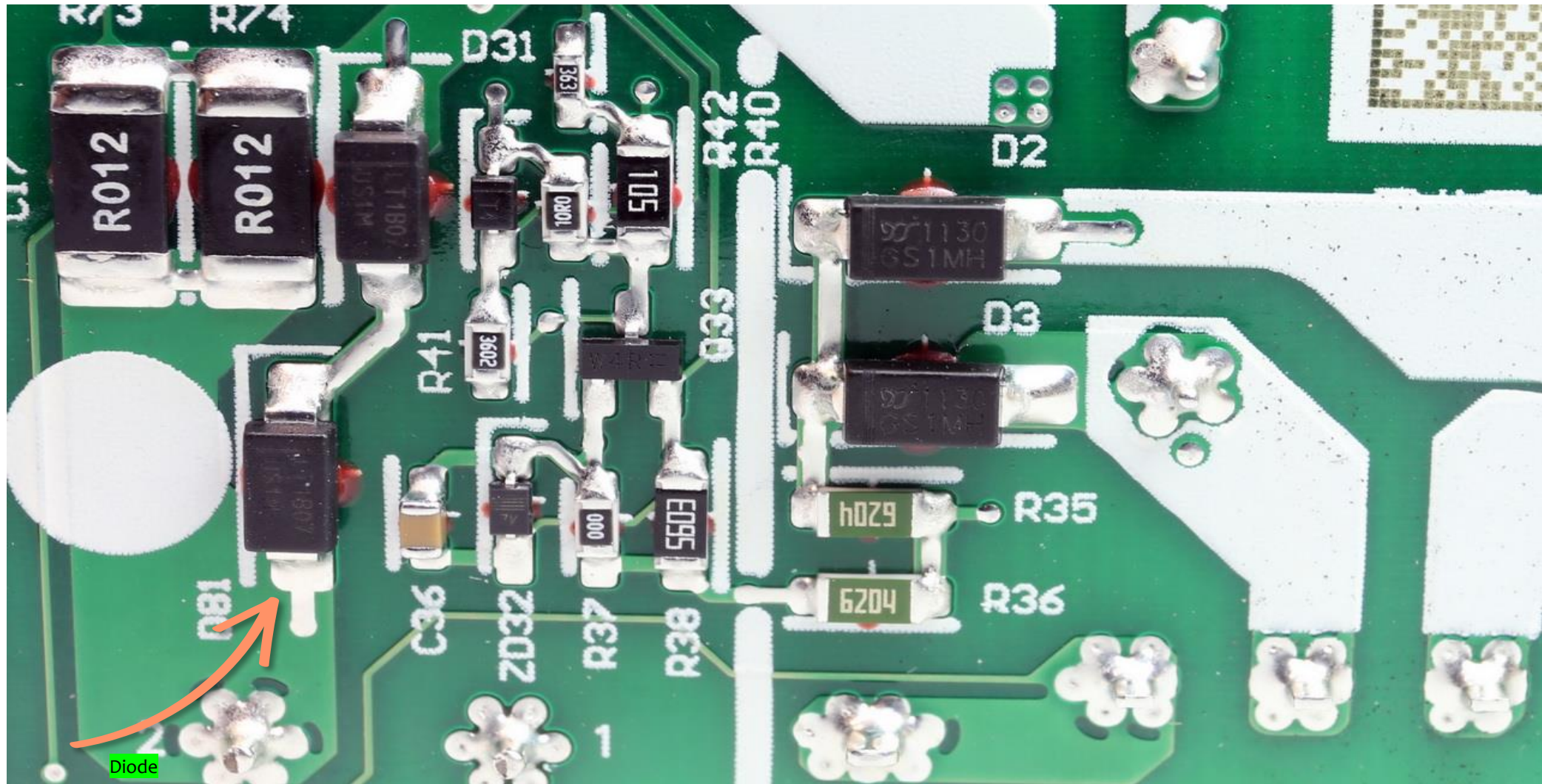Check for shorts and search for burn marks



Fusible resistor



Fusable resistor

A fusible resistor, also known as a fuse resistor or a safety resistor, is a type of resistor that is designed to act as a fuse in case of excessive current or power dissipation. It combines the functions of a resistor and a fuse into a single component.


Resistor has continuity then resistor and is low resistance then it is OK

Resistor has no continuity then resistor is blown.

Also check if the Boost Diode and Mosfet are shorted.

Check the APFC / PWM controller IC, because the IC drives these diode and mosfet for the PFC circuit.

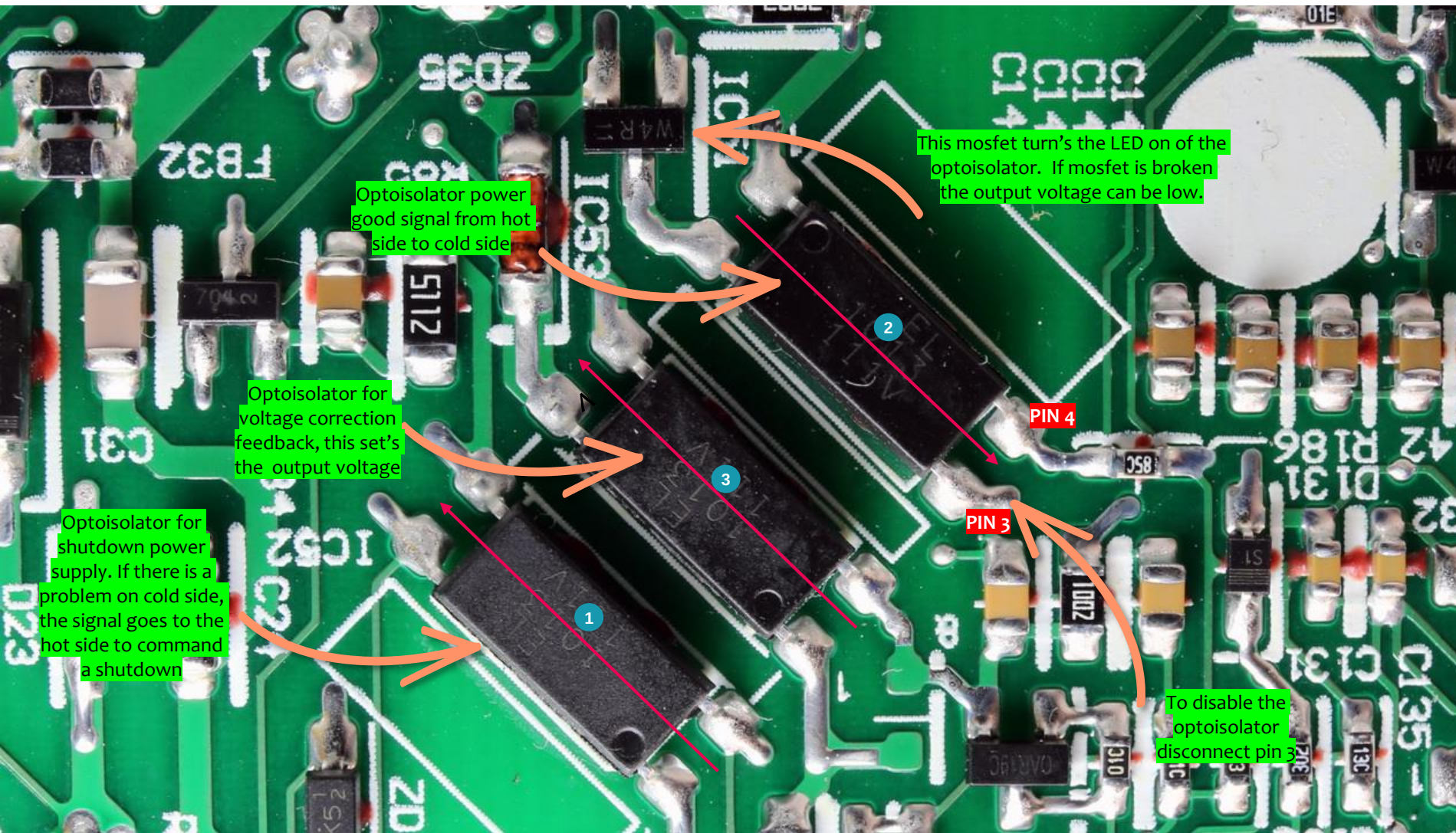Optoisolator for voltage correction feedback




Feedback loop

By using an optoisolator in the feedback loop, the output voltage can be constantly monitored and regulated. Any deviation from the desired voltage will be detected by the optocoupler, allowing the control circuit to make appropriate adjustments.

OUTPUT < +12v check mosfet / optoisolator

If main capacitors voltage is higher then +-390V check if these optoisolator are ok and not leaking.

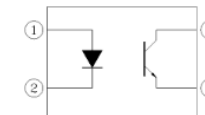Measure the resistance of the collector / emitter junction between pin 3 and 4 of the optoisolator. It should be infinite resistance



Pin Configuration

1. Anode
2. Cathode
3. Emitter
4. Collector